



V2V EDTECH LLP

Online Coaching at an Affordable Price.

OUR SERVICES:

- Diploma in All Branches, All Subjects
- Degree in All Branches, All Subjects
- BSCIT / CS
- Professional Courses



+91 93260 50669



v2vedtech.com



V2V EdTech LLP



v2vedtech



MODEL ANSWER
WINTER- 18 EXAMINATION

Subject Title: Applied Electronics

Subject Code: 22329


3 Hours / 70 Marks


Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more Importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for anyequivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No.	Sub Q.N.	Answer	Marking Scheme
Q.1		Attempt any FIVE of the following :	10-Total Marks
	a)	Define the term related to power amplifier. (i) Efficiency (ii) Voltage gain	2M
	Ans:	<p>(i) <u>Efficiency</u>: Efficiency of the power amplifier is defined as the ratio of maximum a.c. output power to the d.c. input power. Mathematically,</p> <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 10px auto;"> $\% \eta = \frac{P_o(ac)}{P_i(dc)} \times 100\%$ </div> <p>(ii) <u>Voltage gain</u>: Voltage gain of the power amplifier is defined as the ratio of output voltage to the input voltage. Mathematically,</p> <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 10px auto;"> $A_v = \frac{V_{out}}{V_{in}}$ </div>	1 Mark for each definition

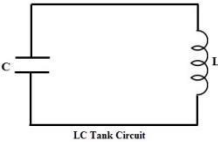

b)	List any four applications of RC coupled amplifier.	2M
Ans:	Applications of RC coupled amplifier: (i) Widely used as Voltage amplifiers. (ii) They are used in Public Address System. (iii) In Tape recorders. (iv) In stereo amplifiers (v) In T.V. V.C.R. and C.D. Players.	1 Marks each (Any four)
c)	State the role of tuned LC circuit in tuned amplifier.	2M
Ans:	<p>In order to pick up and amplify the desired radio frequency signal, the resistive load in the audio amplifier is replaced by a tuned circuit (also called a parallel resonant circuit) as shown in the figure. The tuned circuit is capable of selecting a particular frequency and rejecting the others.</p>  <p>LC Tank Circuit</p> <p>Thus the use of tuned circuit in the transistor amplifier circuit, makes possible the selection and amplification of a particular desired radio frequency. Such an amplifier is called tuned voltage amplifier.</p> <p>Thus an amplifier, which amplifies a specific frequency (or a narrow band frequencies), is called a tuned voltage amplifier or simply tuned amplifier. It serves following two purposes:</p> <p>(i) Selection of desired radio frequency signal.</p> <p>(ii) Amplification of the selected signal to a suitable voltage level.</p>	State 1 ½ Marks and Diagram 1/2 mark
d)	List different types of feedback amplifiers.	2M
Ans:	<u>Types of feedback amplifiers:</u> 1. Positive feedback amplifiers 2. Negative feedback amplifiers (i) voltage series feedback amplifiers (ii) voltage shunt feedback amplifiers (iii) current series feedback amplifiers (iv) current shunt feedback amplifiers	Each type 1 mark
e)	List the advantages of negative feedback over positive feedback.	2M
Ans:	<u>Advantages of negative feedback over positive feedback:</u> 1. Higher fidelity i.e. more linear operation. 2. Highly stabilized gain. 3. Increased bandwidth i.e. improved frequency response.	Any four Each 1 mark

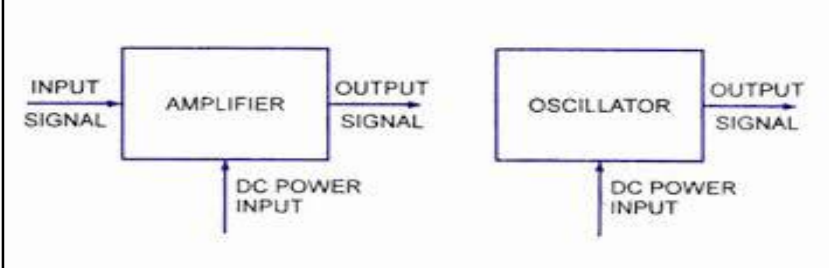
	<p>4. Less amplitude distortion.</p> <p>5. Reduced noise.</p> <p>6. Less harmonics distortion.</p> <p>7. Less phase distortion.</p> <p>8. Input and output impedance can be modified as desired.</p> <p>9. Less frequency distortion.</p>	
f)	Compare amplifier and oscillator.	2M
Ans:	<div style="border: 1px solid black; padding: 10px; margin-bottom: 10px;">  </div> <p>Figure shows a block diagram of an amplifier and an oscillator.</p> <p>An amplifier is a device, which produces an output signal with similar waveform as that of the input. But its power level is generally high. This additional power is supplied by an external D.C. source. Thus an amplifier is essentially an energy convection device I.e. a device, which gets energy from the D.C. source and converts it into an a.c. energy at the same frequency as that of the input signal. The D.C. to A.C.. conversion is controlled by the input signal. It means that if there is no input signal then no energy conversion take place. Thus there is no output signal.</p> <p>An oscillator is a device, which produces an output signal, without any input signal of any desired frequency. It keeps producing an output signal, so long as the D.C. power is supplied. An oscillator does not require any external signal to start or maintain energy conversion process.</p>	Diagram 1 mark and explanation 1 mark
g)	State use of heat sink.	2M
Ans:	<p>Heat sink is a heat exchanger used to transfer heat generated by a <i>mechanical or an electronic device</i> to the surroundings.</p> <p>Heat sinks are either made up of aluminium or copper or any other material which is good conductor of heat. Because conductor helps in conduction of heat from heated surface to the outside air.</p> <p>Heat sinks are commonly used in laptops, computers etc.</p> <p>A heat sink is usually made out of copper and/or aluminum.</p>	State 2 mark

Q 2	Attempt any THREE of the following :	12-Total Marks
a)	<p>Explain with the help of waveforms, the working principle of single stage CE amplifier.</p> <div style="text-align: center; border: 1px solid black; padding: 10px; margin: 10px 0;"> </div> <p>CIRCUIT DESCRIPTION:</p> <ul style="list-style-type: none"> The input a.c. signal is applied across the base emitter terminals of the transistor & output is taken across collector emitter terminals of the transistor. V_{BB} supply forward biases the emitter base junction & V_{CC} supply reverse biases the output junction. The Q point is determined by the V_{CC} supply along with the resistance R_C. The resistances R_1, R_2, R_E form the biasing & stabilization circuit & thus establishes proper operating point. Input capacitor ($C_{in} \approx 10\mu F$): It blocks DC voltage to the base, if it is not provided the source resistance comes across R_2, so that transistor gets unbiased. It allows A.C. to pass & isolates source resistance from R_2. Emitter capacitance ($C_E \approx 100\mu F$): it is used in parallel with R_E to provide a low reactance path to the amplified a.c. signal. If it is not used then amplified a.c. signal flowing through R_E will cause a voltage drop across it, thus reducing the output voltage. Coupling capacitor ($C_C \approx 10\mu F$): it couples one stage of amplification to the next stage. If it is not used, R_C comes across with the R_1 of next stage & biasing of 2nd stage gets disturbed. In short it isolates the d.c. of one stage from the next stage but allows the A.C. signal. <p>PHASE REVERSAL / WORKING:</p> <ul style="list-style-type: none"> Consider above common emitter amplifier circuit. The input a.c. signal is applied across the base emitter terminals of the transistor & output is taken across collector emitter terminals of the transistor. V_{BB} supply forward biases the emitter base junction & V_{CC} supply reverse biases the output junction. Now apply KVL to collector to emitter loop' <p>$V_{CC} - I_C R_C - V_{CE} = 0.$</p>	4M
Ans:	<p style="text-align: right;">Circuit 2 M and explanation 1 M and waveform 1 M</p>	

$\therefore V_{CC} - I_C R_C = V_{CE}$(1)

- When the input a.c. signal voltage increases, the base current increases as a result collector current increases (as $I_C = \beta I_B$). Hence voltage drop $I_C R_C$ increases. As V_{CC} is constant, from equation 1 output voltage V_{CE} decreases.
- From above in common emitter amplifier when the input increases in the positive, the output voltage decreases. i.e. output is 180° out of phase with input.

Waveform:

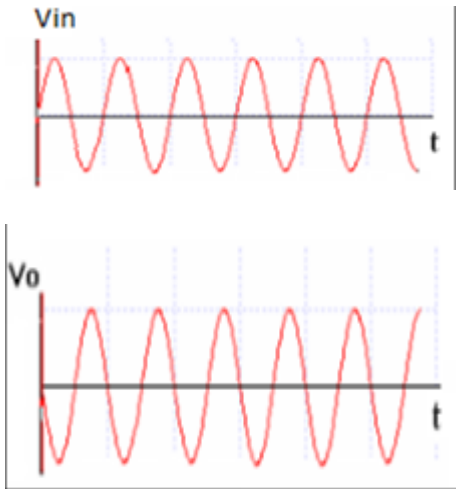

b) Compare positive and negative feedback.


4M

Ans:

Sr. No.	Parameter	Positive feedback	Negative feedback
1	BW	Increases	Decreases
1	Feedback signal	In phase with the input signal.	180° out of phase with the input signal.
2	Net input signal	Increases	Decreases
3	Gain	Increases	Decreases
4	Noise	Increases	Decreases
5	Stability	Poor	Improved
6	Input impedance	decreases	increases
7	Output impedance	increases	decreases
8	Uses	Oscillators, Schmitt trigger	Amplifiers, bootstrapping

Any four points
Each point 1 M

c)	<p>Define oscillator and state the Barkhausen criterion for the generation of sustained oscillations.</p>				4M
Ans:	<p><u>Oscillator</u>: An oscillator is a device, which produces an output signal, without any input signal of any desired frequency.</p> <p><u>Barkhausen criterion</u>: The overall voltage gain of a positive feedback amplifier is given by,</p> <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 10px auto;"> $A' = \frac{A}{1 - \beta A}$ </div> <p style="text-align: right;">.....(1)</p> <p>Where, A = gain of an amplifier without feedback also called open loop gain βA = product of feedback fraction and open loop gain. It is called loop gain.</p> <p>The Barkhausen criterion for the generation of sustained oscillations for positive feedback are:</p> <ol style="list-style-type: none"> 1. $\beta A = 1$ 2. $\angle \beta A = 360^\circ$ or 0° i.e. the total phase shift should be 360° or 0°. 				<p>Definiti on 1 M and Barkhau sen criterion 3 M</p>
d)	<p>Explain the working of SMPS with neat block diagram.</p>				4M
Ans:	<div style="border: 1px solid black; padding: 10px; margin-bottom: 10px;"> </div> <p>A block diagram of Switch Mode Power Supply is shown in figure. The first block is rectifier and filter that converts the A.C. supply voltage to pulsating D.C. which is then filtered out to reduce the amount of ripple content. This section uses the power diodes in bridge configuration to obtain the pulsating d.c. and the capacitor is used as a filter element. The second block is the high frequency switching section and it uses either MOSFETs or BJTs to convert the D.C. voltage to a high frequency ac\c. square wave. This high frequency a.c. square waves ranges from 20 KHz to 100 KHz. Since the power transistors are not operated in their active region, their operation results in low power dissipation. Thus it is a two stage conversion i.e. the input a.c. supply voltage is first rectified to d.c. and then the high frequency switching section changes it back to A.C.</p> <p>The next block of SMPS is high frequency power transformer that isolate the circuit and step up or step down the voltage to the desired voltage level. The output of the transformer is the input of the second rectifier section, called the output rectifier section. This rectifier section is different from the first block of the rectifier in that the frequency of the voltage is very high. Therefore, the bridge configuration of this rectifier uses a high frequency diodes such as schottky diode and the output ripple is naturally filtered because of the number of the overlaps between each individual output pulse. Since the ripple is very</p>				<p>Block diagram 2 M And explanat ion 2 M</p>

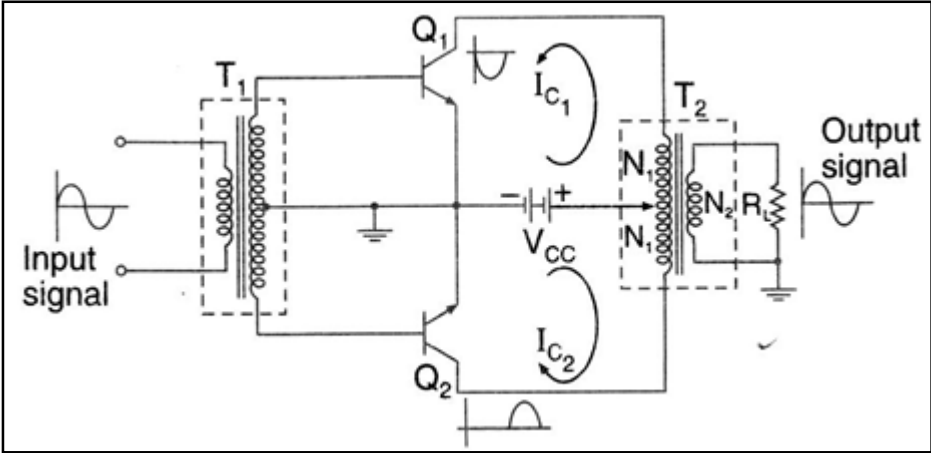
		<p>small in output voltage of the rectifier, a small capacitance is required in the filter section.</p> <p>The last section of the SMPS is the control and feedback block, which contains circuitry that provides Pulse Width Modulation (PWM) output signal. The PWM controller provides duty cycle that varies pulse by pulse to provide an accurate d.c. output voltage.</p>	
Q.3		Attempt any THREE of the following :	12-Total Marks
	a)	Explain with sketch the working of class B push pull amplifier.	4M
	Ans:	<p>Circuit Diagram:-</p>  <p><u>Operation:</u></p> <ul style="list-style-type: none"> • In class B amplifier transistor conduct only for half cycle of input signal. One conduct in positive half cycle and other conducts in negative half cycle. • Transformer T₁ is called as input transformer called phase splitter and produces two signals which are 180 degree out of phase with each other. • Transformer T₂ is called as output transformer and is required to couple the a.c signal from the collector to the load. • When there is no input signals both the transistor Q₁ and Q₂ are cut off hence no current is drawn from V_{cc} supply. Thus there is no power wasted in stand by the power dissipation in both transistor is practically zero. • During positive half cycle ON Q₂ OFF and at the output half cycle is obtained Q₁ during negative half OFF and Q₂ on hence another half cycle is obtained cycle Q₁ at the output. • Then output transformer joins these two halves and produces a full sine wave in the load resistor. 	Circuit Diagram 2M & Operati on 2M
	b)	Compare different types of power amplifier on basis of- (i) Efficiency.	4M

	(ii) Power dissipation in transistor. (iii) Conduction angle of collector current (iv) Position of Q.																										
Ans:	<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 20%;">Parameter</th> <th style="width: 20%;">Class A</th> <th style="width: 20%;">Class B</th> <th style="width: 20%;">Class AB</th> <th style="width: 20%;">Class C</th> </tr> </thead> <tbody> <tr> <td>Position of operating pt. (Q Point) on load line</td> <td>Q point is at the center of load line.</td> <td>On X axis</td> <td>Just above X axis.</td> <td>Below X axis.</td> </tr> <tr> <td>Efficiency</td> <td>lowest efficiency 25% to 50%</td> <td>Above 78.5%</td> <td>Between 50 to 78.5%</td> <td>Above 95%</td> </tr> <tr> <td>Conduction Angle of collector current</td> <td>Conducts for (360⁰) full cycle of input signal</td> <td>(180⁰) half cycle of input signal.</td> <td>Greater than 180⁰ and less than 360⁰</td> <td>Less than 180⁰ of input signal.</td> </tr> <tr> <td>Power dissipation in transistor</td> <td>Very High</td> <td>Low</td> <td>Low</td> <td>Very Low</td> </tr> </tbody> </table>	Parameter	Class A	Class B	Class AB	Class C	Position of operating pt. (Q Point) on load line	Q point is at the center of load line.	On X axis	Just above X axis.	Below X axis.	Efficiency	lowest efficiency 25% to 50%	Above 78.5%	Between 50 to 78.5%	Above 95%	Conduction Angle of collector current	Conducts for (360 ⁰) full cycle of input signal	(180 ⁰) half cycle of input signal.	Greater than 180 ⁰ and less than 360 ⁰	Less than 180 ⁰ of input signal.	Power dissipation in transistor	Very High	Low	Low	Very Low	Each difference carry 1M
Parameter	Class A	Class B	Class AB	Class C																							
Position of operating pt. (Q Point) on load line	Q point is at the center of load line.	On X axis	Just above X axis.	Below X axis.																							
Efficiency	lowest efficiency 25% to 50%	Above 78.5%	Between 50 to 78.5%	Above 95%																							
Conduction Angle of collector current	Conducts for (360 ⁰) full cycle of input signal	(180 ⁰) half cycle of input signal.	Greater than 180 ⁰ and less than 360 ⁰	Less than 180 ⁰ of input signal.																							
Power dissipation in transistor	Very High	Low	Low	Very Low																							
c)	Draw miller sweep generation and give its applications.		4M																								
Ans:	<p><u>Diagram:</u></p> <p style="text-align: center;">(a) Miller sweep circuit.</p> <p><u>Applications of Miller Sweep Generator:</u> (any two)</p> <ol style="list-style-type: none"> 1. Applications where linear output is expected. 2. Television (TV) 3. CRO 4. To convert step waveform into ramp waveform. 	Diagram: 2M & Applications (any two) 2M																									

d)


Sketch the circuit diagram for dual voltage regulator using IC 78XX and 79XX to obtain $\pm 12V$ output.

4M

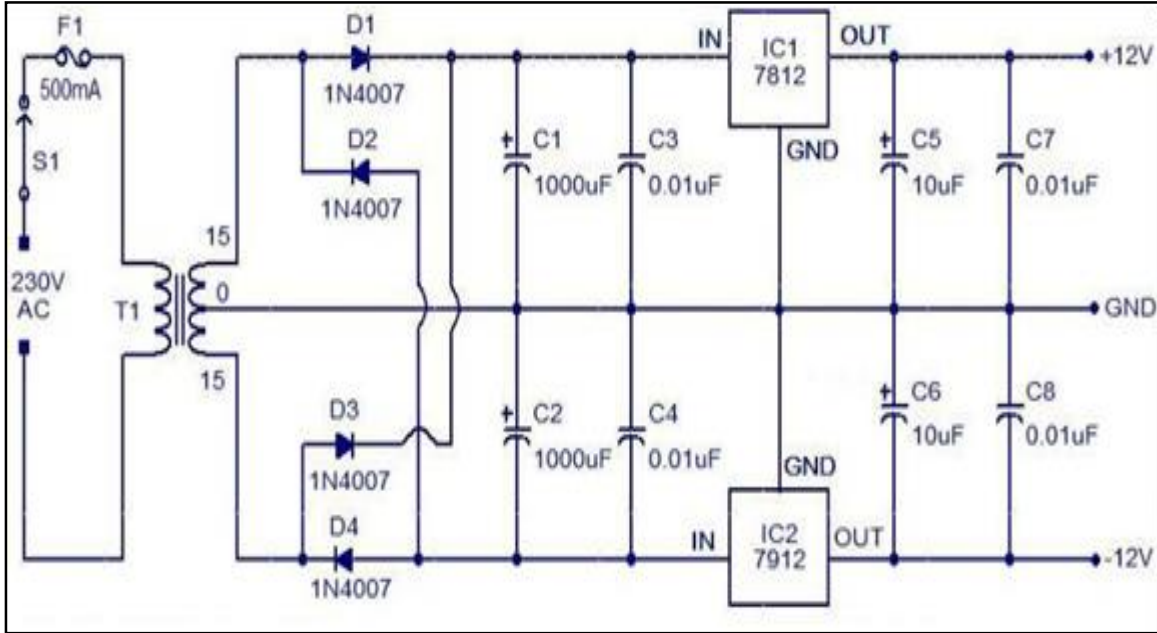

OR

Ans:

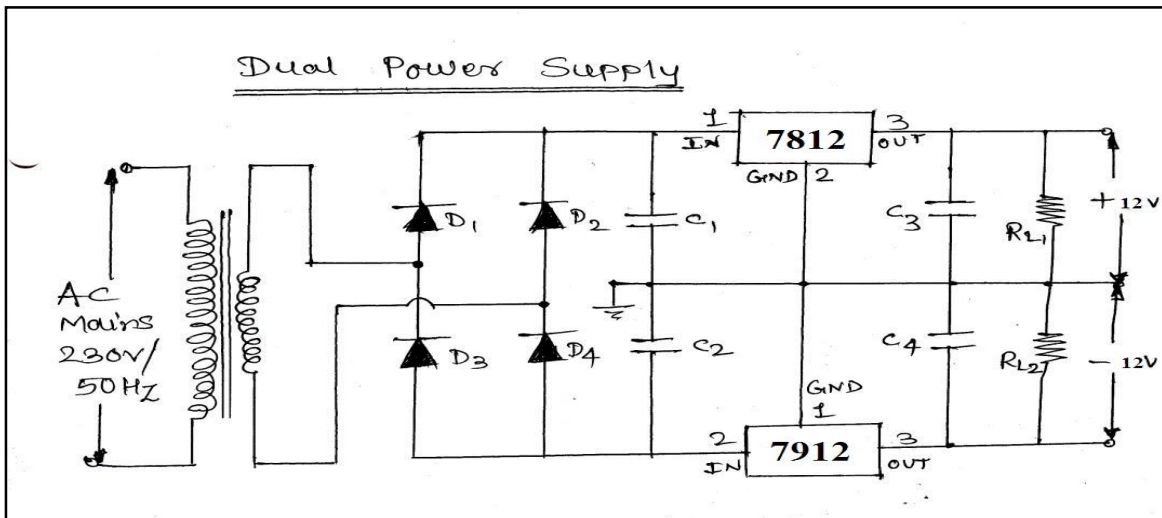

Q.4	A)	Attempt any THREE of the following :	12-Total Marks
	a)	<p>State the necessity of regulated power supply. Define load and line regulation.</p> <p><u>Necessity of regulated power supply: 2M</u></p> <p>The major disadvantage of a power supply is that the output voltage changes with the variations in the input voltage or The D.C output voltage of the rectifier also increase similarly, In many electronic applications, it is desired that the output voltage should remain constant regardless of the variations in the input voltage or load. In order to get ensure this; a voltage stabilizing device called voltage regulator is used.</p> <p><u>Load Regulation: 1M</u></p> <p>The load regulation indicates the change in output voltage that will occur per unit change in load current. Mathematically,</p> $\text{Load Regulation} = \frac{V_{NL} - V_{FL}}{\Delta I_L}$ <p>Where, V_{FL} is full load voltage ΔI_L is change in load current V_{NL} is no load voltage</p> <p><u>Line Regulation: 1M</u></p> <p>The change in output voltage with respect to per unit change in input voltage is defined as line regulation. It is mathematically expressed as,</p> $\text{Line regulation} = \Delta V_L / \Delta V_S$ <p>Where, ΔV_L = The change in output voltage ΔV_S = The change in input voltage</p>	4M
	Ans:	<p style="text-align: right;">Necessity 2M , Load Regulation 1M & Line regulation 1M</p>	
	b)	<p>Explain the working principle of crystal oscillator with diagram.</p> <p><u>Circuit Diagram:</u></p>	4M
	Ans:		



Working Principle of Piezoelectric Crystal:

- A Quartz Crystal has a very peculiar property known as Piezoelectric Effect.
- According to this effect, when an AC voltage is applied across a quartz crystal, it vibrates at a frequency of applied voltage.
- Conversely, if a mechanical force is applied to vibrate a quartz crystal it generates an AC voltage.
- Above fig shows the circuit of crystal oscillator using transistor. In this circuit, the crystal is connected as a series element in the feedback path from collector to the base.
- The resistors R₁, R₂ and R_E provide voltage divider stabilized d.c. bias circuit. The capacitor C_E provides a.c bypass of emitter resistor and RFC coil provides for d.c bias. The coupling capacitor C has negligible impedance at the circuit operating frequency.
- The circuit frequency of oscillation is set by the series resonant frequency of the crystal and its value is given by the relation

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

Or

Working Principle:

When the D.C. power is switched on, the noise voltage of small amplitude appearing at the base gets amplified and appears at the output. This amplified noise now drives the feedback network consisting of a quartz crystal and capacitor C. Thus the crystal is excited by a fraction of energy feedback from the output to the input. The crystal is made to operate as an inductor L so that the feedback network consists of series resonant LC circuit. This is possible only, if the frequency of oscillations f₀ is in between the series resonant frequency f_s and the parallel resonant frequency f_p of an electrical equivalent circuit of a crystal. Thus, the frequency of oscillations is set by the series resonant frequency f_s of the crystal. This produces undamped oscillations of stable frequency f₀.

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

c) Compare the performance of current series and current shunt feedback amplifier. 4M


	Sr.No.	Characteristics	Current series feedback amplifier	Current shunt feedback amplifier	
Ans:	1.	Voltage gain	Decreases	Decreases	(Any Four) each carry 1M
	2.	Bandwidth	Increases	Increases	
	3.	Harmonic distortion	Decreases	Decreases	

4.	Noise	Decreases	Decreases
5.	Input resistance	Increases	Decreases
6.	Output resistance	Increases	Increases

d) Describe with help of circuit diagram working of class A power amplifier.

4M

Circuit Diagram:

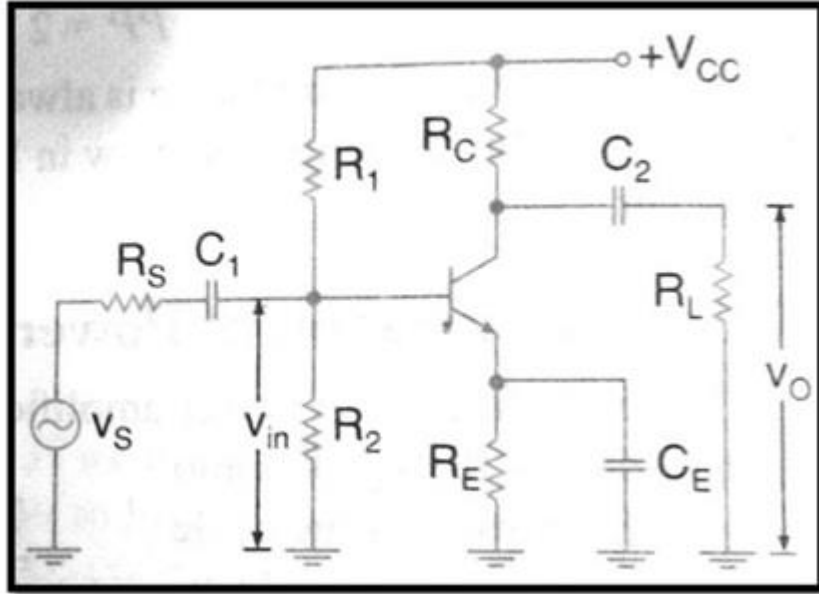

Working:

Ans:

The input a.c. signal is applied across the base emitter terminals of the transistor & output is taken across collector emitter terminals of the transistor. V_{BB} supply forward biases the emitter base junction & V_{CC} supply reverse biases the output junction.

The Q point is determined by the V_{CC} supply along with the resistance R_C . The resistances R_1, R_2, R_E form the biasing & stabilization circuit & thus establishes proper operating point.


Input capacitor ($C_{in} \approx 10\mu F$) : It blocks DC voltage to the base, if it is not provided the source resistance comes across R_2 , so that transistor gets unbiased. It allows ac to pass & isolates source resistance from R_2 .

Class A amplifier is basically, a common emitter amplifier. This circuit is called direct coupled class A power amplifier. The only difference between this circuit and small signal version, considered earlier, is that the signals handled by the power amplifier circuit are in the range of volt.

Or

Circuit Diagram:

Circuit Diagram 2M & Working 2M

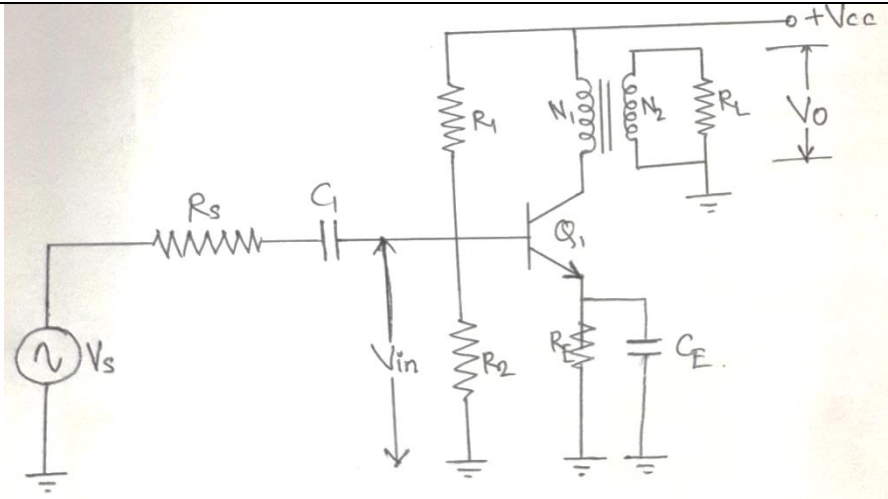

e) Compare single tuned and double tuned amplifier with respect to operating principle, frequency response, efficiency and applications.


Sr.No.	Characteristics	Single tuned amplifier	Double tuned amplifier
1.	Operating Principle	Parallel Resonance	Parallel Resonance
2.	Frequency response		
3.	Efficiency	High	Low
4.	Application	TRF receiver, TV receiver	IF amplifier in Radio receiver, TV receiver

Ans:

Q.5	Attempt any TWO of the following :	12- Total Marks
a)	Explain with diagram the working of phase shift oscillator. Also a phase shift oscillator has $R = 220\text{ k}\Omega$ and $C = 500\text{ pf}$. Calculate the frequency of sine wave generated by the oscillator.	6M
Ans:	<p><u>Circuit Diagram of RC PHASE SHIFT OSCILLATOR:</u></p> <div style="text-align: center;"> </div>	Circuit Diagram: 2M Working: 2M Calculation for $f_o = 2M$
	OR	



	<p><u>WORKING:</u></p> <ul style="list-style-type: none"> • Common emitter amplifier introduces a 180° phase shift between input & output. & remaining 180° phase shift is produced by three identical basic RC phase shifting networks. • Each RC network is designed to introduce a phase shift of 60°. • The phase shift around the loop is 360° only at one precise frequency. • This frequency of oscillation is given by $f_o = \frac{1}{2 \pi RC \sqrt{6}}$ <ul style="list-style-type: none"> • The feedback factor $\beta = \frac{1}{29}$ • Therefore $A_V = 29$ <p>Calculation For f_o: Given: R= 220 KΩ C= 500pF To Find: Frequency of oscillation f_o. Formula Used: $f_o = \frac{1}{2 \pi RC \sqrt{6}}$ Solution: $f_o = \frac{1}{2 \pi RC \sqrt{6}}$</p> $f_o = \frac{1}{2 \pi * 220K\Omega * 500pF * \sqrt{6}}$ <p>$f_o = 590.67$ Hz</p> <p>The frequency of sine wave generated by the oscillator = 590.67 Hz.</p>	
b)	Explain operation of FET common source amplifier with applications.	6M
Ans:	<p>COMMON SOURCE FET AMPLIFIER: <u>Circuit Diagram:</u></p>	<p>Circuit Diagram: 2M Operation: 2M Applications (any 2): 2M</p>

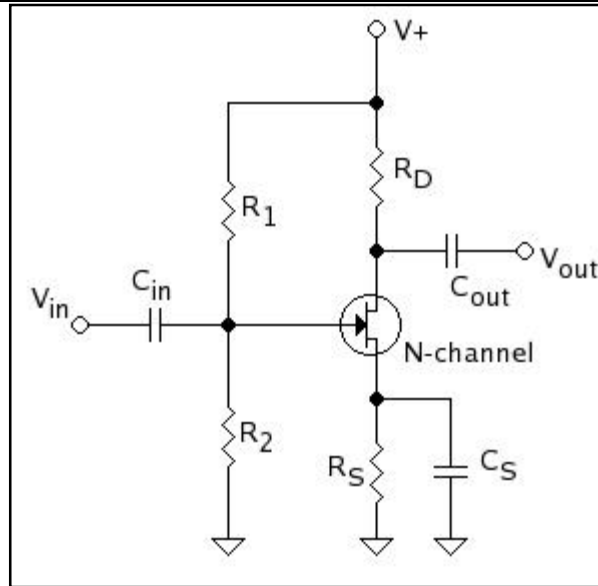

- Above circuit shows CS N-channel FET amplifier.
- Voltage divider biasing circuit is used.
- C_1 & C_2 are coupling capacitors used to couple input AC signal & output respectively.
- C_S is a bypass capacitor which keeps the source of FET effectively.

OPERATION:

DURING POSITIVE HALF CYCLE:

- As the gate to source voltage increases, the drain current also increases.
- As a result of this, the voltage drop across resistor R_D also increases.
- This causes the drain voltage to decrease. As $V_{DS} = V_{DD} - I_D R_D$.
- It means that the positive half cycle of the input produces negative half cycle of the output voltage.
- In other words output voltage is 180 out of phase with the input voltage.

DURING NEGATIVE HALF CYCLE:


- As the gate to source voltage decreases, the drain current also decreases.
- As a result of this, the voltage drop across resistor R_D also decreases.
- This causes the drain voltage to increase. As $V_{DS} = V_{DD} - I_D R_D$.
- It means that the negative half cycle of the input produces positive half cycle of the output voltage.
- In other words output voltage is 180 out of phase with the input voltage.

APPLICATIONS OF CS-FET AMPLIFIER:

- As a pre-amplifier in audio circuits.
- As a voltage amplifier.
- In the public address system.
- In radio & TV amplifier circuit.

c)	<p>Explain with circuit diagram and waveform the operation of class AB push pull power amplifier</p>	6M
	<p>Class AB Push Pull Power Amplifier: Circuit Diagram:</p> <div style="text-align: center;"> </div> <p>Circuit Description: The circuit consists of two centre-tapped transformers T_1 and T_2, two identical transistors Q_1 and Q_2, Resistor R and diode D. The DC voltage developed across the diode D is connected to the bases of both the transistors through the secondary winding of the input transformer. This voltage acts as DC bias for the transistors because it is equal to cut-in voltage and they will conduct for complete half cycle period of the input to eliminate the cross-over distortion.</p> <p>WORKING:</p> <p>Ans:</p> <ul style="list-style-type: none"> ➤ When there is no a.c. input signal is applied both the transistors Q_1 & Q_2 are cut off. Hence no current is drawn from V_{CC}. ➤ DURING POSITIVE HALF CYCLE: <ul style="list-style-type: none"> • The base of the transistor Q_1 is positive and that of Q_2 is negative. • As a result of this Q_1 conducts, while the transistor Q_2 is OFF. ➤ DURING NEGATIVE HALF CYCLE: <ul style="list-style-type: none"> • The base of the transistor Q_2 is positive and that of Q_1 is negative. • As a result of this Q_2 conducts, while the transistor Q_1 is OFF. ➤ Thus at any instant any one transistor in the circuit is conducting. ➤ Then the output transformer joins these two halves & produces a full sine wave in the load resistor. 	<p>Circuit Diagram: 2M Operation: 2M Waveform: 2M</p>

		<p><u>Waveform:</u></p> <div style="text-align: center;"> <p style="text-align: center;">Class AB Amplifier Operation</p> </div>	
Q.6	Attempt any TWO of the following:		12- Total Marks
	a)	Explain stagger tuned amplifier with the help of waveforms.	6M
Ans:	<p><u>Circuit Diagram:</u></p> <div style="text-align: center;"> </div> <p>Above figure shows two-stage tuned voltage amplifier. The stagger tuning in this circuit, may be achieved by resonating the tuned circuits L_1C_1 and L_2C_2 to slightly different frequencies.</p> <p><u>Frequency Response:</u></p>		<p>Circuit Diagram: 2M Waveform (Frequency Response): 2M Explanation: 2M</p>

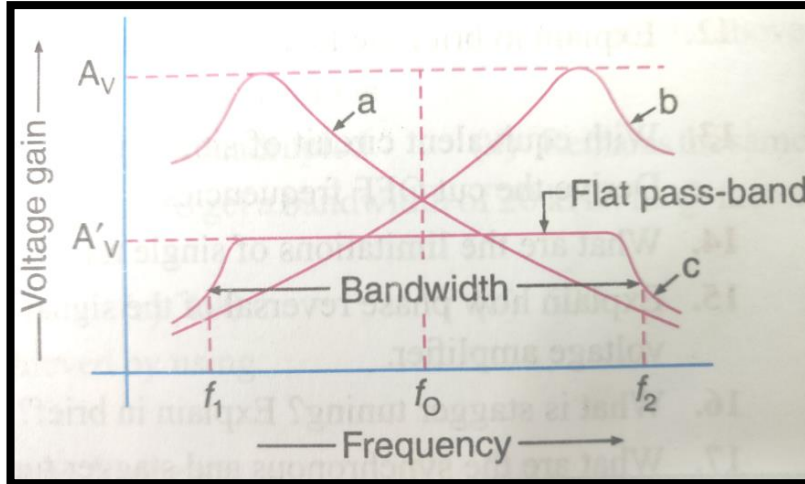


Above figure shows frequency response of a stagger-tuned amplifier. In this figure, curve 'a' shows the gain versus frequency of the L_1C_1 tuned circuit. Similarly the curve 'b' shows the response of the L_2C_2 tuned circuit. The curve 'c' indicates the combined response of the circuit. It is evident from this curve that the amplifier has a greater bandwidth and flatter pass-band. It has been found that more the number of stages used, flatter will be the pass-band and steeper will be the gain fall-off outside the pass-band. Because of the stagger tuning there is a loss of voltage gain.

b) Draw the circuit of complementary, symmetry push pull amplifier and explain its working.

6M

COMPLEMENTRY SYMMETRY CLASS B PUSH PULL AMPLIFIER

Circuit Diagram:

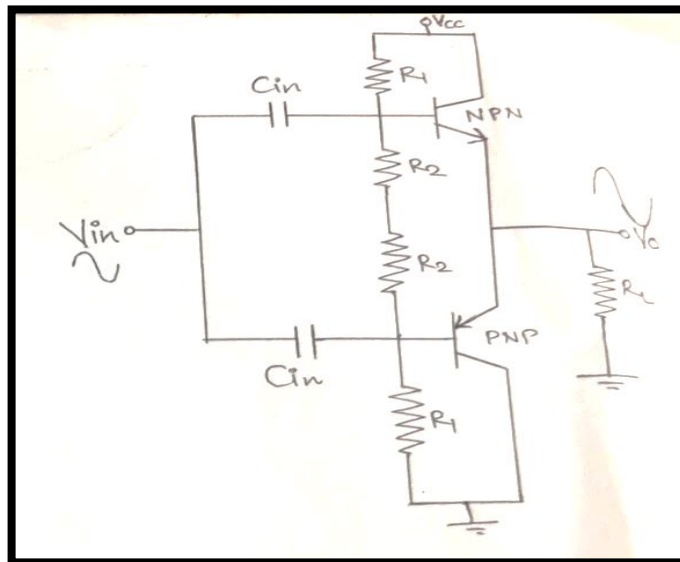

Ans:

Circuit description:

- Two transistors one NPN & other PNP is used in the circuit so they are complementary to each other.
- Biasing conditions used for both transistors are same so they are symmetrical.
- R_1, R_2, V_{CC} are used for voltage divider bias of transistors.
- Both transistors conduct for 180° as it is class B amplifier.
- Whenever one transistor is ON other push to be OFF so the name push pull.

Circuit diagram : 2m
Circuit description: 1m
Working: 2m
Waveform: 1m



	<p>Working:</p> <ul style="list-style-type: none">➤ Input signal V_{in} is applied to both the transistor through input capacitor.➤ During positive half cycle of input:<ul style="list-style-type: none">• The base of the transistors NPN & PNP is positive.• As a result of this NPN conducts & PNP remains OFF.• So we get half cycle in the output.➤ During negative half cycle of input:<ul style="list-style-type: none">• The base of the transistors NPN & PNP is negative.• As a result of this PNP conducts & NPN remains OFF.• So we get remaining half cycle in the output.	
c)	<p>In voltage amplifier output voltage without negative feedback is 10V. If 25% of output voltage its feedback in series with input voltage. Find Feedback voltage, also give value of the feedback factor.</p>	6M
Ans:	<p>Given Data: $V_{OUT} = 10V$ 25% of output voltage its feedback in series with input voltage.</p> <p>To find:</p> <ol style="list-style-type: none">1. Feedback voltage V_F2. Feedback factor β <p>Solution:</p> <ol style="list-style-type: none">1. Feedback voltage V_F: 25% of output voltage its feedback in series with input voltage. i.e. $V_F = 25\%$ of V_{OUT} $V_F = 25\%$ of 10V $V_F = 2.5V$2. Feedback factor β: $\beta = \frac{V_F}{V_{OUT}}$ $\therefore \beta = \frac{2.5V}{10V}$ $\therefore \beta = 0.25$ <div style="border: 1px solid black; padding: 5px; width: fit-content; margin-top: 10px;"><ol style="list-style-type: none">1. Feedback voltage $V_F = 2.5V$2. Feedback factor $\beta = 0.25$</div>	<p>Calculation of feedback voltage: 3m Calculation of feedback factor: 3m</p>



V2V EDTECH LLP

Online Coaching at an Affordable Price.

OUR SERVICES:

- Diploma in All Branches, All Subjects
- Degree in All Branches, All Subjects
- BSCIT / CS
- Professional Courses



+91 93260 50669



v2vedtech.com



V2V EdTech LLP



v2vedtech



MODEL ANSWER

SUMMER- 19 EXAMINATION

Subject Title: Applied Electronics Subject Code: 22329

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more Importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No.	Sub Q.N.	Answer	Marking Scheme
Q.1		Attempt any Five :	10M
	a)	State classification of Amplifiers.	2M
	Ans:	<p>CLASSIFICATION OF AMPLIFIERS:</p> <p>A] Based on input signal</p> <ol style="list-style-type: none"> 1. Small signal amplifiers 2. Large signal amplifiers <p>B] Based on output signal</p> <ol style="list-style-type: none"> 1. Voltage amplifier 2. Power amplifier <p>C] Based on biasing conditions</p> <ol style="list-style-type: none"> 1. Class A amplifier 2. Class B amplifier 3. Class AB amplifier 4. Class C amplifier <p>D] Based on frequency response</p> <ol style="list-style-type: none"> 1. Audio frequency amplifier 2. Radio frequency amplifier <p>E] Based on coupling</p> <ol style="list-style-type: none"> 1. Direct coupled amplifiers 2. R-C Coupled amplifier 	2M




	3. Transformer coupled amplifier	
b)	Define the terms related to tuned amplifiers (i) Resonant Frequency(Fr) (ii) Q Factor	2M
Ans:	(i) Resonant Frequency(Fr): It is a frequency at which the inductive reactance is equal to the capacitive reactance i.e. $X_L=X_C$ (ii) Q Factor: The quality factor or Q factor is a measure of the performance of a coil, capacitor inductor in terms of its losses and resonator bandwidth. $Q_0 = \frac{X_L}{R} = \frac{\omega_0 L}{R} = \frac{2\pi f_0 L}{R}$ Where , L = value of circuit inductance. R = Value of circuit resistance.	1M 1M
c)	State the need of multistage amplifier.	2M
Ans:	Need of multistage amplifier: The voltage (or power) gain, obtained from a single stage small signal amplifier, is limited. Therefore, it is not sufficient for all practical applications. Therefore, in order to obtain greater voltage and power gain, we have to use more than one stage of amplification. Such an amplifier is called a 'MULTISTAGE AMPLIFIER'.	2M
d)	List the types of power amplifiers.	2M
Ans:	Types of power amplifiers:- 1. Class A amplifier 2. Class B amplifier 3. Class AB amplifier 4. Class C amplifier	Each type: 1/2M
e)	List advantages of negative feedback(any four)	2M
Ans:	Advantage of negative feedback amplifier: <ul style="list-style-type: none">• Increased stability in gain• Increased bandwidth• Less amplitude and harmonic distortion• Decreased noise• Less frequency distortion• Less non-linear distortion• Input and output resistance can be modified as desired.	Each point: 1/2M
f)	Define : (i) Sweep time (ii) Retrace time	2M
Ans:	(i) Sweep time: It is defined as time interval taken by time based signal generator to increase from minimum to maximum voltage.	1M

		<p>(ii) Retrace time: It is defined as time taken by time based signal generator to decrease from maximum to minimum voltage.</p>	1M																																				
	g)	State fixed voltage regulator IC'S.	2M																																				
	Ans:	<p>Fixed voltage regulator IC's can provide fixed amount of voltage either in positive or in negative. 78XX can generate positive values of voltages. E.g.</p> <table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>IC NUMBER</th> <th>OUTPUT VOLTAGE</th> </tr> </thead> <tbody> <tr><td>7805</td><td>+5.0 V</td></tr> <tr><td>7806</td><td>+6.0 V</td></tr> <tr><td>7808</td><td>+8.0 V</td></tr> <tr><td>7809</td><td>+9.0 V</td></tr> <tr><td>7812</td><td>+12.0 V</td></tr> <tr><td>7815</td><td>+15.0 V</td></tr> <tr><td>7818</td><td>+18.0 V</td></tr> <tr><td>7824</td><td>+24.0 V</td></tr> </tbody> </table> <p>79XX can generate negative values of voltages.</p> <table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>IC NUMBER</th> <th>OUTPUT VOLTAGE</th> </tr> </thead> <tbody> <tr><td>7905</td><td>-5.0 V</td></tr> <tr><td>7906f</td><td>-6.0 V</td></tr> <tr><td>7908</td><td>-8.0 V</td></tr> <tr><td>7909</td><td>-9.0 V</td></tr> <tr><td>7912</td><td>-12.0 V</td></tr> <tr><td>7915</td><td>15.0 V</td></tr> <tr><td>7918</td><td>-18.0 V</td></tr> <tr><td>7924</td><td>-24.0 V</td></tr> </tbody> </table>	IC NUMBER	OUTPUT VOLTAGE	7805	+5.0 V	7806	+6.0 V	7808	+8.0 V	7809	+9.0 V	7812	+12.0 V	7815	+15.0 V	7818	+18.0 V	7824	+24.0 V	IC NUMBER	OUTPUT VOLTAGE	7905	-5.0 V	7906f	-6.0 V	7908	-8.0 V	7909	-9.0 V	7912	-12.0 V	7915	15.0 V	7918	-18.0 V	7924	-24.0 V	<p>Any two IC's from 78XX & 79XX series ½ M each</p>
IC NUMBER	OUTPUT VOLTAGE																																						
7805	+5.0 V																																						
7806	+6.0 V																																						
7808	+8.0 V																																						
7809	+9.0 V																																						
7812	+12.0 V																																						
7815	+15.0 V																																						
7818	+18.0 V																																						
7824	+24.0 V																																						
IC NUMBER	OUTPUT VOLTAGE																																						
7905	-5.0 V																																						
7906f	-6.0 V																																						
7908	-8.0 V																																						
7909	-9.0 V																																						
7912	-12.0 V																																						
7915	15.0 V																																						
7918	-18.0 V																																						
7924	-24.0 V																																						
Q 2		Attempt any Three of the following :	12M																																				
	a)	Sketch circuit diagram of RC coupled single stage CE amplifier. State the function of each component.	4M																																				
	Ans:	<p>Circuit diagram of RC coupled single stage CE amplifier:</p> <p style="text-align: center;">Single stage RC coupled CE amplifier</p> <p>Function of Components:</p> <ul style="list-style-type: none"> The Q point is determined by the V_{CC} supply along with the resistance R_C. The resistances R_1, R_2, R_E form the biasing & stabilization circuit. Thus establishes proper operating point. Input capacitor ($C_{in} \approx 10\mu F$): It blocks DC voltage to the base, if it is not provided the source resistance comes across R_2, so that transistor gets unbiased. It allows a.c. to pass & isolates source resistance from R_2. Emitter capacitance ($C_E \approx 100\mu F$): it is used in parallel with R_E to provide a low 	<p>2M</p> <p style="text-align: right;">Each component function: 1/2 M</p>																																				

		<p>reactance path to the amplified a.c. signal. If it is not used then amplified a.c. signal flowing through R_E will cause a voltage drop across it, thus reducing the output voltage.</p> <ul style="list-style-type: none"> • Coupling capacitor ($C_C \approx 10\mu F$): it couples one stage of amplification to the next stage. If it is not used, R_C comes across with the R_1 of next stage & biasing of 2nd stage gets disturbed. In short it isolates the d.c. of one stage from the next stage but allows the a.c. signal. 	
	b)	Describe the working of single stage class A amplifier with circuit diagram	4M
	Ans:	Circuit diagram of single stage class A amplifier:	2M
		<p style="text-align: center;">Figure (a) OR</p> <p style="text-align: center;">Figure (b)</p>	
		<p>Working:-</p> <p>For figure (a):-</p> <ul style="list-style-type: none"> • This is the simplest type of Class A power amplifier circuit. • It uses a single-ended transistor for its output stage with the resistive load connected directly to the Collector terminal. When the transistor switches “ON” it sinks the output current through the Collector resulting in an inevitable voltage drop across the Emitter resistance thereby limiting the negative output capability. • The efficiency of this type of circuit is very low (less than 30%) and delivers small power outputs for a large drain on the DC power supply. • A Class A amplifier stage passes the same load current even when no input signal is 	2M

		<p>applied so large heat sinks are needed for the output transistors.</p> <p>For Figure (b):- An output transformer improves the efficiency of the amplifier by matching the impedance of the load with that of the amplifiers output impedance. By using an output or signal transformer with a suitable turns ratio, class-A amplifier efficiencies reaching 40% are possible.</p>	
	c)	Explain principle of feedback amplifier.	4M
	Ans:	<p>Block diagram of feedback amplifier:-</p> <div style="text-align: center;"> </div> <p>Explanation:-</p> <ul style="list-style-type: none"> • “Feedback” is a process of injecting some energy from the output and then it back to the input. The amplifier which use the feedback principle are called feedback amplifier“. • Depending upon whether the feedback signal increases or decreases the input signal, there are 2 basic types of feedback: Positive feedback and Negative feedback. <p>From the above figure, the gain of the amplifier is represented as A. the gain of the amplifier is the ratio of output voltage V_o to the input voltage V_i. The feedback network extracts a voltage $V_f = \beta V_o$ from the output V_o of the amplifier.</p> <p>This voltage is added for positive feedback and subtracted for negative feedback, from the signal voltage V_s. Now,</p> $V_i = V_s + V_f$ $= V_s + \beta V_o \dots \dots \dots \text{for Positive feedback}$ $V_i = V_s - V_f$ $= V_s - \beta V_o \dots \dots \dots \text{for Negative feedback}$ <p>The quantity $\beta = V_f/V_o$ is called as feedback ratio or feedback fraction.</p>	2M
	d)	Draw circuit diagram of RC phase shift oscillator and state its working.	4M
	Ans:	Circuit diagram of RC phase shift oscillator:	2M

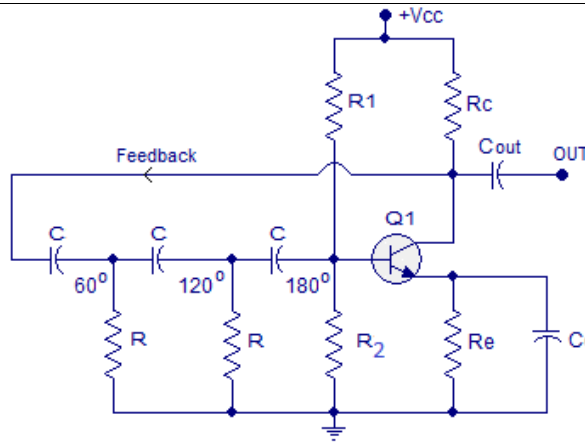

WORKING:

- Circuit consists of a single stage amplifier in common emitter configuration & RC phase shifting network.
- R_1, R_2, R_E provides biasing & C_E is bypass capacitor.
- Common emitter amplifier introduces a 180° phase shift between input & output. & remaining 180° phase shift is produced by three identical basic RC phase shifting networks.
- Each RC network is designed to introduce a phase shift of 60° .
- The phase shift around the loop is 360° only at one precise frequency.
 - This frequency of oscillations is equal to $\frac{1}{2\pi RC\sqrt{6}}$
 - The feedback factor $\beta = \frac{1}{29}$
 Therefore $A_v = 29$.

2M

Q.3

Attempt any three:


12-
Total
Marks

a)

Sketch circuit diagram of common source FET Amplifier. State working principle of it.

4M

Ans:

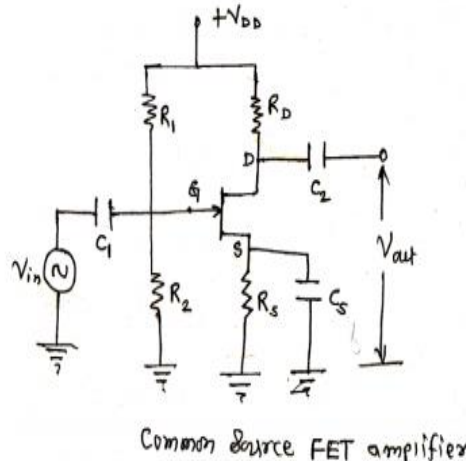

2M

Working: -

- When small a.c. signal is applied to the gate, it produces variation in

2M

	<p>the gate to source voltage. This produces variation in the drain current. As the gate to source voltage increases, the drain current also increases. As the result of this voltage drop across R_D also increases. This causes the drain voltage to decreases.</p> <ul style="list-style-type: none"> As the input voltage rises, gate to source voltage becomes less negative, it will increase the channel width and increase the level of drain current I_D. As the input voltage falls, it will decrease the channel width and decrease the level of drain current I_D. Thus I_D varies sinusoidally above its Q point value. The drain to source voltage V_{DS} is given by $V_{DS} = V_{DD} - I_D R_D$ Therefore as I_D increases the voltage drop $I_D R_D$ will also increase and voltage V_{DS} will decrease. If ΔI_D is large for a small value of ΔV_{GS}; the ΔV_{DS} will also be large and we get amplification. Thus the AC output voltage V_{DS} is 180° out of phase with AC input voltage. 	
b)	Explain the term crossover distortion. State methods to overcome it.	4M
Ans:	<p>Explanation:-</p> <ul style="list-style-type: none"> Cross over distortion occurs in Class B push pull Amplifier. In the push-pull configuration, the two identical transistors get into conduction, one after the other and the output produced will be the combination of both. When the signal changes or crosses over from one transistor to the other at the zero voltage point, it produces an amount of distortion to the output wave shape. For a transistor in order to conduct, the base emitter junction should cross $0.7V$, the cut off voltage. The time taken for a transistor to get ON from OFF or to get OFF from ON state is called the transition period. At the zero voltage point, the transition period of switching over the transistors from one to the other, has its effect which leads to the instances where both the transistors are OFF at a time. Such instances can be called as Flat spot or Dead band on the output wave shape. <p>Waveform:-</p> <p style="text-align: center;">Output waveform</p> <p>Method to overcome :</p> <p>This cross over distortion can be eliminated if the conduction of the amplifier is more than</p>	<p>2M</p> <p>1M</p> <p>1M</p>

one half cycle, so that both the transistors won't be OFF at the same time. The remedy is to use Class AB amplifier.


c) Compare positive feedback and negative feedback on the basis of:
 (i) **Gain**
 (ii) **Bandwidth**
 (iii) **Phase shift**
 (iv) **Stability**

Ans:

Sr. no.	Parameter	Positive feedback	Negative feedback
1	Gain	Increases	Decreases
2	Bandwidth	Decreases	Increases
3	Phase shift	0 or 360 degree	180 degree
4	Stability	Poor	Improved

d) Draw block diagram of SMPS. State its working principle.

Ans: Block diagram of SMPS:-

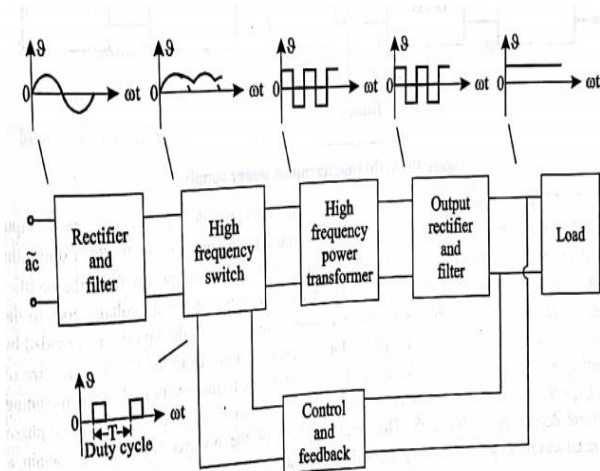

Working principle:-

A switched-mode power supply is an electronic power supply that incorporates a switching regulator to convert electrical power efficiently.


An SMPS transfers power from a DC or AC source (often mains power) to DC loads, such as a personal computer, while converting voltage and current characteristics. Unlike a linear power supply, the pass transistor of a switching-mode supply continually switches between low-dissipation, full-on and full-off states, and spends very little time in the high dissipation transitions, which minimizes wasted energy.



Ideally, a switched-mode power supply dissipates no power.

Voltage regulation is achieved by varying the ratio of on-to-off time.

2M

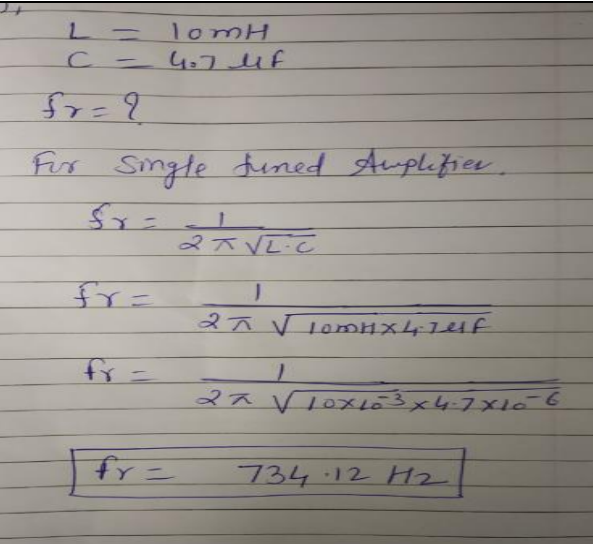


		<p>Switching regulators are used as replacements for linear regulators when higher efficiency, smaller size or lighter weights are required.</p> <p style="text-align: center;">OR</p> <p>Working :-</p> <p>Rectifier and filter :- It converts the ac supply voltage to a pulsating dc, which is then filtered out to reduce the amount of ripple content. It uses the power diodes in a bridge configuration to obtain the pulsating dc and the capacitor is used as a filter element.</p> <p>High-frequency switching:- It uses either MOSFETs or BJTs to convert the dc voltage to high frequency ac square wave. This high-frequency ac square wave ranges from 20 kHz to 100 kHz. Since the power transistors are not operated in their active region, their operation results in low power dissipation. Thus, it is a two stage conversion. i.e. the input ac supply voltage is first rectified to dc and then the high- frequency switching section changes it back to ac.</p> <p>High frequency power transformer:-It isolates the circuit and steps-up or steps-down the voltage to the desired voltage level. The output of the transformer is the input of the second rectifier section, called the output rectifier section.</p> <p>Output rectifier :- This rectifier section is different from the first block of the rectifier in that the frequency of the voltage is very high. Therefore, the bridge configuration of this rectifier uses a high frequency diode such as a Schottky diode and the output ripple is naturally filtered because of the number of overlaps between each individual output pulse. Since the ripple is very small in the output voltage of the rectifier, a small capacitance value is required in the filter section.</p> <p>Control and feedback:- It provides a pulse width modulation(PWM) output signal. The PWM controller provides a duty-cycle that varies pulse by pulse to provide an accurate dc output voltage.</p>	
Q.4	A)	Attempt any THREE of the following :	12- Total Marks
	a)	Calculate Resonant frequency of single tuned amplifier, if inductor L = 10mH and Capacitor C = 4.7 μf of tank circuit.	4M
	Ans:	 <p> $L = 10\text{mH}$ $C = 4.7\ \mu\text{F}$ $f_r = ?$ For single tuned Amplifier, $f_r = \frac{1}{2\pi\sqrt{L \cdot C}}$ $f_r = \frac{1}{2\pi\sqrt{10\text{mH} \times 4.7\ \mu\text{F}}}$ $f_r = \frac{1}{2\pi\sqrt{10 \times 10^{-3} \times 4.7 \times 10^{-6}}}$ $f_r = 734.12\ \text{Hz}$ </p>	<p>Form ula & unit 1M</p> <p>each Corret ans 2M</p>

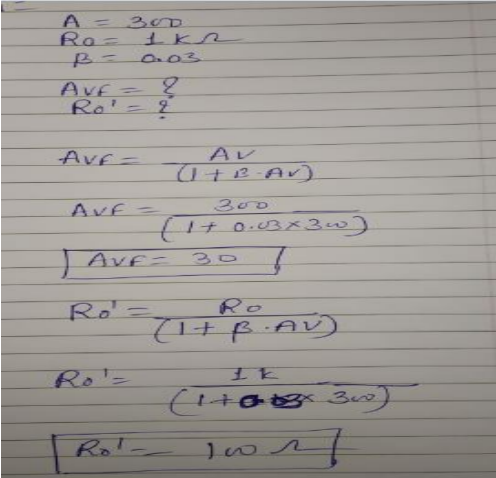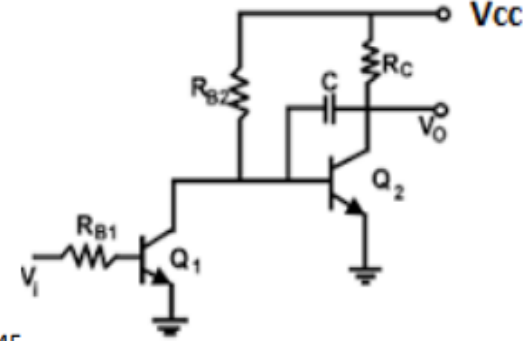b)	<p>An amplifier has gain 'A' of 300 without feedback, output impedance is $1K\Omega$. If negative feedback with feedback factor 0.03 is introduced in the circuit then calculate the gain with feedback and output impedance of this feedback amplifier.</p>		4M
Ans:	 <p> $A = 300$ $R_o = 1K\Omega$ $\beta = 0.03$ $A_{vf} = ?$ $R_{o'} = ?$ $A_{vf} = \frac{AV}{(1 + \beta \cdot AV)}$ $A_{vf} = \frac{300}{(1 + 0.03 \times 300)}$ $A_{vf} = 30$ $R_{o'} = \frac{R_o}{(1 + \beta \cdot AV)}$ $R_{o'} = \frac{1K}{(1 + 0.03 \times 300)}$ $R_{o'} = 100\Omega$ </p>		<p>gain with feedback- 2M, output impedance- 2M</p>
c)	<p>Describe miller sweep generator circuit with neat input output waveforms</p>		4M
Ans:	<p>Circuit diagram:-</p>  <p style="text-align: right;">2M</p> <p>Working:</p> <ul style="list-style-type: none"> • Figure shows the circuit of a Miller integrator or a sweep circuit. • Transistor Q_1 acts as a switch and transistor Q_2 is a common - emitter amplifier. i.e. a high gain amplifier. • Consider the case when Q_1 is ON and Q_2 is OFF. At this condition, the voltage across the capacitor C and the output voltage V_o is equal to V_{cc}. • When a negative pulse is applied to the base of Q_1, the emitter - base junction of Q_1 is reverse biased and hence Q_1 is turned OFF. 		1M

- Thus, the collector voltage (V_{c1}) of Q_1 increases which increases the bias to Q_2 and as a result Q_2 is turned ON. Since Q_2 conducts, V_o begins to decrease. Because the capacitor is coupled to the base of transistor Q_2 , the rate of decrease of output voltage is controlled by rate of discharge of capacitor. The time constant of the discharge is given by $t_d = R_{B2} * C$.
- As the value of time constant is very large, the discharge current practically remains constant. Hence, the rundown of the collector voltage is linear. When the input pulse is removed, Q_1 turns ON and Q_2 turns OFF. The capacitor charges quickly to $+V_{cc}$ through R_c with the time constant $t = R_c * C$

1M

Waveform:

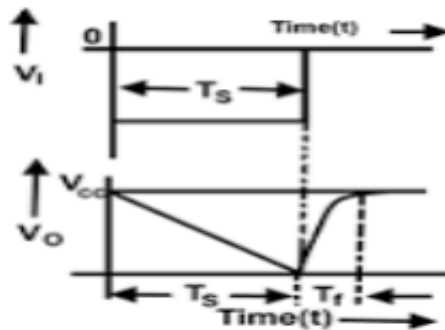


d) Describe block diagram of IC 723 regulator. State the working principle of IC723.

4M

Ans:

Block diagram of IC 723 regulator:-

2M

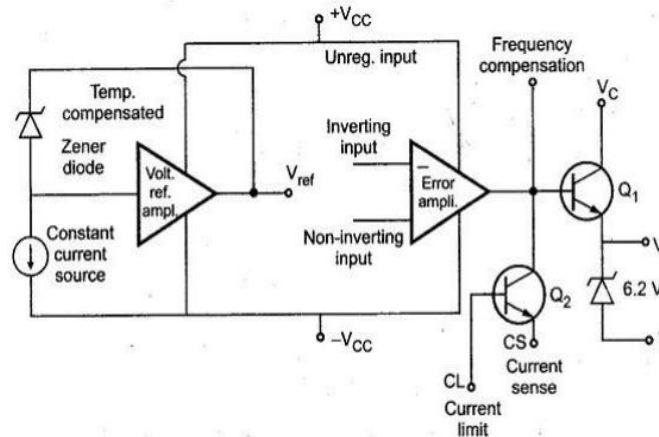

Working principle:-

- It consists of a voltage reference source, an error amplifier, a series pass transistor and a current limiting transistor.
- The device can provide voltage with an output voltage ranging from 2 V to 37 V, and output current levels up to 150 m A.

2M



		<ul style="list-style-type: none"> • The working can be explained by dividing it into two blocks, the reference voltage generator and the error amplifier. • In the reference voltage generator, a Zener diode is being compelled to operate at fixed point (so that sneer output voltage is a fixed voltage) by a constant current Source which comes along with an amplifier to generate a constant voltage of 7.15V at the Verve pin of the IC. • As for the error amplifier section, it consists of an error amplifier, a series pass transistor Q1 and a current limiting transistor. • The error amplifier can be used to compare the output voltage applied at Inverting input terminal through a feedback to the reference voltage Verve applied at the Non-Inverting input terminal. This connection is not provided internally and so has to be externally provided in accordance with the required output voltage. • The conduction of the transistor Q1 is controlled by the error signal. It is this transistor that controls the output voltage. 	
--	--	---	--


Q.5	Solve any TWO :	12M
------------	------------------------	------------

	a)	<p>Compare RC coupled, transformer coupled, direct Coupled amplifier on the basis of:</p> <ul style="list-style-type: none"> (i) Type of coupling (ii) Frequency response (iii) Gain (iv) Application 	6M
--	----	--	-----------

Ans:		Sr. no	Parameter	RC coupling	Transformer coupling	Direct coupling	1 ½ M each point
		1	Types of coupling	RC coupling-Resistor, Capacitor are used as a coupling network	Transformer is used as a coupling network	No coupling network is u	
		2	Frequency Response				




	3	Gain	Overall gain is less due to loading effect	It provides high voltage gain than RC coupled	Uniform gain up to certain frequency, gain rolls off at high frequency	
	4	Application	Voltage amplification	Power amplification	Low frequency amplification	
b)	<p>A complementary symmetry pushpull amplifier is operated using ± 10 volt and deliver power to load $R_L=50$. Calculate.</p> <p>i) Maximum power output ii) Power rating of transistor iii) D.C input at maximum power output.</p>					6M
Ans:	<p>Given : $V_{cc} = \pm 10V$ $R_L = 50\Omega$.</p> <p>i) Maximum Power output. $P_o(\max) = \frac{V_{cc}^2}{2 \cdot R_L} = \frac{(10)^2}{2 \times 50} = \frac{100}{100} = 1W.$</p> <p>ii) Power rating of transistor $V_m = \frac{2V_{cc}}{\pi} = \frac{2}{\pi} \times 10 = 6.36V.$ <p>Total collector power rating in two transistor $P_c(dc) = P_{in}(dc) - P_o(ac)$ $= V_{cc} \left(\frac{2V_m}{\pi \cdot R_L} \right) - \left(\frac{V_m^2}{2R_L} \right)$ $= 10 \left(\frac{2 \times 6.36}{\pi \times 50} \right) - \frac{(6.36)^2}{2 \times 50}$ $= 0.8097 - 0.4044$ $= 0.4053 W.$ <p>Power rating of each transistor $= \frac{P_c(dc)}{2} = \frac{0.4053}{2} = 0.2026 W.$</p> <p>iii) D.C i/p at maximum power output $P_{in}(dc)_{\max} = V_{cc} \times \frac{2V_{cc}}{\pi R_L}$ $= 10 \times \frac{2 \times 10}{\pi \times 50}$ $= 1.273 W.$</p></p></p>					2M each point
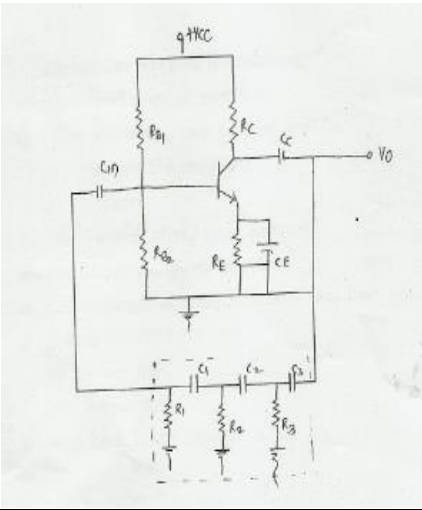
<p>c)</p>	<p>Identify the circuit given in Figure No.1. Calculate output frequency of the given circuit if $R_1=R_2=R_3=2K\Omega$ and $G = C_2=C_3=0.1\mu f$.</p> 	<p>6M</p>
<p>Ans:</p>	<p>The given circuit diagram is RC phase shift Oscillator</p> <p>Given $R_1=R_2=R_3=2K\Omega$ $C_1=C_2=C_3=0.1\mu F$.</p> $freq = \frac{1}{2\pi\sqrt{6} RC}$ $= \frac{1}{2\pi\sqrt{6} \times 2 \times 10^3 \times 0.1 \times 10^{-6}}$ $= 324.87 \text{ Hz.}$	<p>2M</p> <p>2M Formula</p>
<p>Q.6</p>	<p>Attempt any TWO of the following:</p>	<p>12- Total Marks</p>
<p>a)</p>	<p>Compare Class A, Class B, Class C and class AB power amplifiers on the basis of:</p> <p>i) Angle of conduction ii) Efficiency iii) Position of operating point and power dissipation iv) Distortion</p>	<p>6M</p>

		v)Application					
Ans:	Sr. No	Parameter	Class A	Class B	Class C	Class AB	Efficiency point 2M & others points 1M each
	1	Angle of conduction	360^0	180^0	Less than 180^0	More than 180^0 less than 360^0	
	2	Efficiency	25% can increase to 50%	78.5%	95%	78.5%	
	3	Position of operating point in power dissipation	At the center of load line	On X-axis	Below X-axis	Just above X-axis	
	4	Distortion	No distortion	Distortion more than A and AB but less than C	Maximum distortion	Less than B and C but more than A	
	5	Application	Outdoor musical system	Audio power amplifiers	Audio power amplifier	RF amplifier	
b)	Draw Bootstrapped sweep generator circuit. Compare Miller Integrator and bootstrapped sweep generator with respect to the technique used.					6M	
Ans:	Circuit diagram of bootstrap sweep generator:					2M	
Sr. No	Miller Integrator	Bootstrap sweep generator			Any 4 points 1M each		
1	It is an integrator used to convert input step waveform into ramp waveform.	In Bootstrap time base generator a constant current is obtained by maintaining nearly constant voltage across fixed resistor in series with capacitor					
2	In Miller sweep polarity of sweep voltage is negative.	In Bootstrap polarity of sweep voltage is positive					
3	The inverting amplifier is used in this circuit	The non-inverting amplifier is used in this circuit					

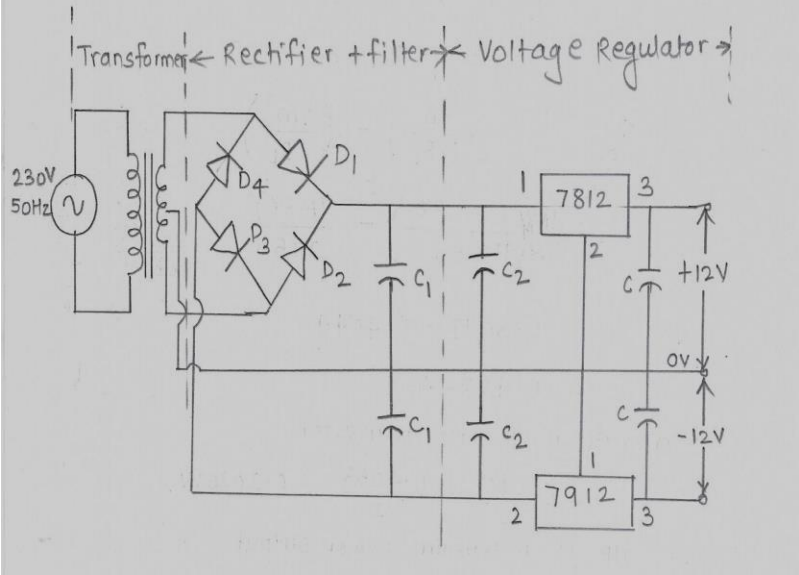

		4	Open circuit gain of the amplifier is infinity	Open circuit gain of the amplifier is unity	
		5	The Linearity of sweep voltage is better than Bootstrap sweep circuit	The linearity of sweep voltage is poor than Miller integrator	
c)	Build the circuit diagram of dual voltage regulator to get +12Vdc and -12Vdc using IC 7812 and IC 7912 along with rectifier.				6M
Ans:					Labeling 2M & correct diagram 4M



V2V EDTECH LLP

Online Coaching at an Affordable Price.

OUR SERVICES:

- Diploma in All Branches, All Subjects
- Degree in All Branches, All Subjects
- BSCIT / CS
- Professional Courses



+91 93260 50669



v2vedtech.com



V2V EdTech LLP



v2vedtech



WINTER – 19 EXAMINATION

Subject Name: Applied Electronics

Model Answer Subject Code:

22329

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No.	Sub Q. N.	Answer	Marking Scheme																				
Q.1		Attempt any FIVE of the following:	10-Total Marks																				
	a)	List the types of coupling used in BJT amplifier.	2M																				
	Ans:	Types of coupling used in BJT amplifier: i. Resistance capacitance (RC) coupling ii. Impedance coupling iii. Transformer coupling iv. Direct coupling	Each ½ M																				
	b)	Compare small signal amplifier with power amplifier (any four)	2M																				
	Ans:	<table border="1"> <thead> <tr> <th>Sr.No</th> <th>Parameters</th> <th>Small signal Amplifiers</th> <th>Power Amplifiers</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>Amplification quantity</td> <td>It increases voltage into high resistance load. Hence small signal amplifiers are also called as voltage amplifiers.</td> <td>It increases power into low resistance load. Hence these amplifiers are also called as large signal amplifiers.</td> </tr> <tr> <td>2</td> <td>Current Gain(β)</td> <td>High (typically 100)</td> <td>Low (5 to 20)</td> </tr> <tr> <td>3</td> <td>Input Resistance(R_i)</td> <td>Quite low</td> <td>Very large</td> </tr> <tr> <td>4</td> <td>Output</td> <td>High</td> <td>low</td> </tr> </tbody> </table>	Sr.No	Parameters	Small signal Amplifiers	Power Amplifiers	1	Amplification quantity	It increases voltage into high resistance load. Hence small signal amplifiers are also called as voltage amplifiers.	It increases power into low resistance load. Hence these amplifiers are also called as large signal amplifiers.	2	Current Gain(β)	High (typically 100)	Low (5 to 20)	3	Input Resistance(R_i)	Quite low	Very large	4	Output	High	low	Any four points: each ½ M
Sr.No	Parameters	Small signal Amplifiers	Power Amplifiers																				
1	Amplification quantity	It increases voltage into high resistance load. Hence small signal amplifiers are also called as voltage amplifiers.	It increases power into low resistance load. Hence these amplifiers are also called as large signal amplifiers.																				
2	Current Gain(β)	High (typically 100)	Low (5 to 20)																				
3	Input Resistance(R_i)	Quite low	Very large																				
4	Output	High	low																				



				Impedance(R_o)				
			5	Physical size	Small	Large in size		
			6	Coupling	R-C coupling	Transformer coupling		
			7	Power output	low	High		
	c)	State four advantages of negative feedback used in feedback amplifier.					2M	
	Ans:	Advantages of negative feedback: (Any Four) i. Distortion decreases ii. Noise in output decreases iii. Stability of gain of amplifier improves iv. It is used as an amplifier. v. Operating point is stabilized. vi. Input resistance increases in certain configuration and output resistance decreases in certain configurations. vii. Bandwidth is increased					Each ½ M	
	d)	State Barkhausen criteria of oscillation.					2M	
	Ans:	Where, A_v = gain of an amplifier without feedback also called open loop gain βA_v = product of feedback fraction and open loop gain. It is called loop gain. The Barkhausen criterion for the generation of sustained oscillations. for positive feedback are: 1. $\beta A = 1$ 2. Total phase shift should be 360° or 0°					1M 1M	
	e)	Differentiate positive feedback and negative feedback (four points)					2M	
	Ans:		Sr. No.	Parameter	Positive feedback	Negative feedback	Any Four points Each ½ M	
			1	Feedback signal	In phase with the input signal.	180° out of phase with the input signal.		
			2	Net input signal	Increases	Decreases		
			3	Gain	Increases	Decreases		
			4	Noise Increases	Increases	Decreases		
			5	Stability	Poor	Improved		
			6	Input impedance	decreases	increases		
			7	Output impedance	increases	decreases		
			8	Uses	Oscillators, Schmitt trigger	Amplifiers, bootstrapping		

	f) State the need of tuned amplifier in electronic circuits.(four points)	2M
Ans:	(Note:Any two points can be given full marks) Need of tuned amplifier: i. Selects the desired radio frequency signal. ii. Amplifies the selected high or radiosignal to a suitable voltage level. iii. As a filter.	2M
	g) List the uses of heat sink (four points)	2M
Ans:	Uses of heat sink: i. It is used to avoid thermal runaway in electronic circuits. ii. Use to transfer heat generated by a mechanical or an electronic device to the surroundings. iii. Use to optimize the heat exchange between component and surrounding by maximizing the contact surface between heat sink and air. iv. Used to dissipate the amount of heat generated.	Each point ½ M

Q.2	Attempt any THREE of the following:	12-Total Marks
	a) Explain the working principle of FET amplifier and list its two applications.	4M
Ans:	<p>Circuit diagram:</p> <p>Explanation:</p> <ol style="list-style-type: none"> When small a.c. signal is applied to the gate, it produces variation in the gate to source voltage. This produces variation in the drain current. As the gate to source voltage increases, the drain current also increases. As the result of this voltage drop across R_D also increases. This causes the drain voltage to decrease. As the input voltage rises, gate to source voltage becomes less negative, it will increase the channel width and increase the level of drain current I_D. As the input voltage falls, it will decrease the channel width and decrease the level of drain current I_D. Thus I_D varies sinusoidally above its Q point value. The drain to source voltage V_{DS} is given by $V_{DS} = V_{DD} - I_D R_D$ Therefore as I_D increases the voltage drop $I_D R_D$ will also increase and voltage V_{DS} will decrease. If ΔI_D is large for a small value of ΔV_{GS}; the ΔV_{DS} will also be large and we get amplification. Thus the AC output voltage V_{DS} is 180° out of phase with AC 	<p>Circuit diagram: 1 ½M</p> <p>1 ½M</p>



input voltage.
Applications: (Any 2)

- i. Low noise amplifier
- ii. Buffer amplifier
- iii. Cascade amplifier
- iv. Analog switch
- v. Multiplexer
- vi. Chopper
- vii. Current limiter

**1M
(1/2 M each)**

b) Compare the performance of voltage series and current series type of negative feedback amplifiers.(four points)

4M


Ans:	Sr.No	Parameters	voltage series negative feedback amplifiers	current series type of negative feedback amplifiers	Any four point Each point
	1	Block diagram			-1M
	2	Gain	Decreases	Decreases	
	3	Output resistance	Decrease $Z_{if} = \frac{Z_i}{1 + \beta A}$	Increase $Z_{if} = Z_i(1 + \beta A)$	
	4	Input resistance	Increases $Z_{if} = Z_i(1 + \beta A)$	Increase $Z_{if} = Z_i(1 + \beta A)$	
	5	Disortion	Decrease	Decrease	

c) Draw the block diagram of SMPS and state its working principle.

4M

Ans: Diagram:

2M

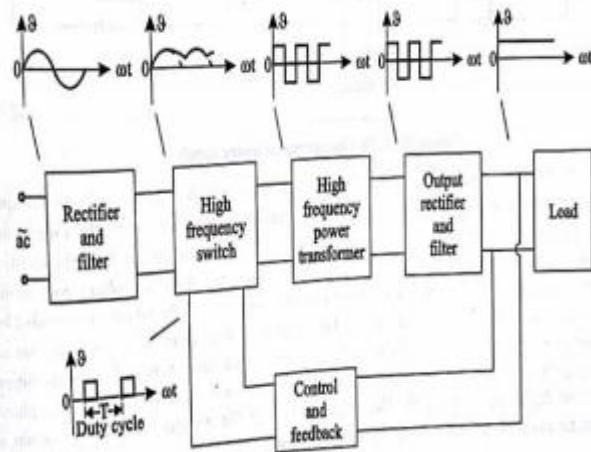

Working principle:-

2M

Rectifier and filter:- It converts the ac supply voltage to a pulsating dc, which is then filtered out to reduce the amount of ripple content. It uses the power diodes in a bridge configuration to obtain the pulsating dc and the capacitor is used as a filter element.

High-frequency switching:- It uses either MOSFETs or BJTs to convert the dc voltage to high frequency ac square wave. This high-frequency ac square wave ranges from 20 kHz to 100 kHz. Since the power transistors are not operated in their active region, their operation results in low power dissipation. Thus, it is a two stage conversion. i.e. the input ac supply voltage is first rectified to dc and then the high-frequency switching section changes it back to ac.

High frequency power transformer:-It isolates the circuit and steps-up or steps-down the voltage to the desired voltage level. The output of the transformer is the input of the second rectifier section, called the output rectifier section.

Output rectifier: - This rectifier section is different from the first block of the rectifier in that the frequency of the voltage is very high. Therefore, the bridge configuration of this rectifier uses a high frequency diode such as a Schottky diode and the output ripple is naturally filtered because of the number of overlaps between each individual output pulse. Since the ripple is very small in the output voltage of the rectifier, a small capacitance value is required in the filter section.


Control and feedback:- It provides a pulse width modulation(PWM) output signal. The PWM controller provides a duty-cycle that varies pulse by pulse to provide an accurate dc output voltage.

d) **Design a RC phase shift oscillator to generate the frequency of 500KHz. Assume suitable values for $R_1=R_2=R_3=R$ and $C_1=C_2=C_3=C$.Justify your answer.**


4M

Ans: **RC Phase shift oscillator:**

**Circuit diagram
1M**

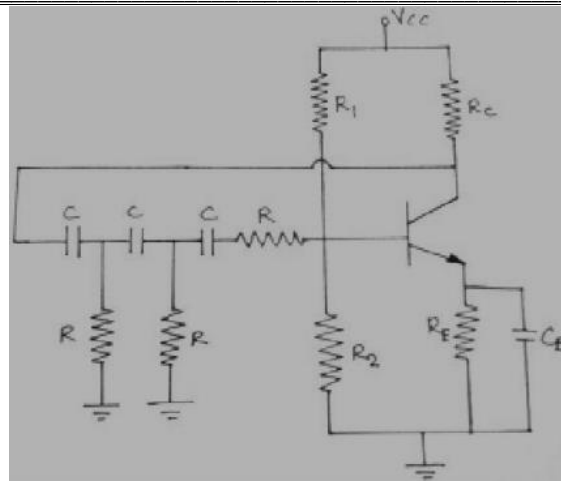

OR

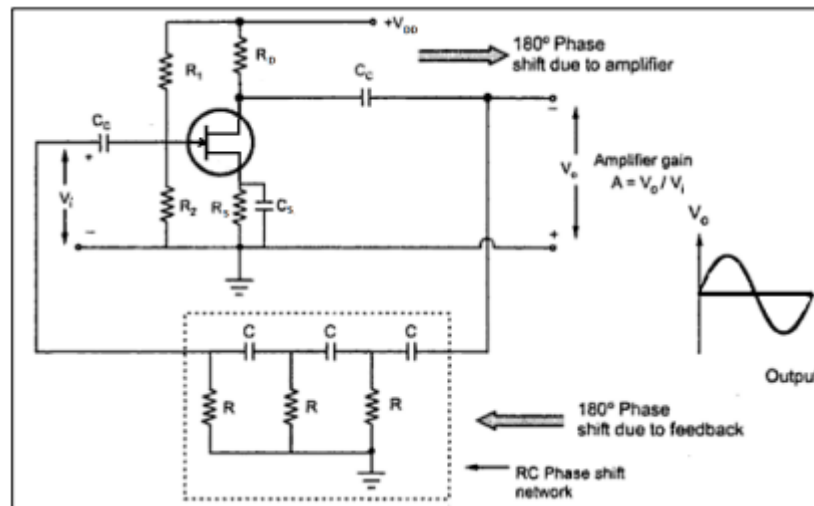


Assume the values of R and C:

(NOTE:STUDENT CAN ASSUME ANY VALUES OF R AND CALCULATE "C" OR ASSUME ANY VALUES "C" AND CALCULATE "R")

Assume

$R_1=R_2=R_3=R=10K\Omega$

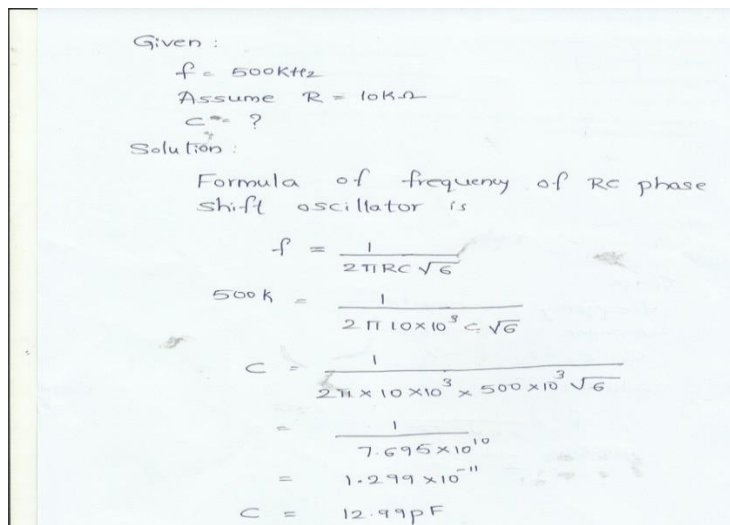

Similarly students can calculate R assuming C

This oscillator is used to generate low frequency signal.


Calculation
2M

Justificatio
n
1M

echoes.

- Current Time base generators produce very high frequency sawtooth waves specifically designed to deflect the beam in cathode ray tube (CRT) smoothly across the face of the tube and then return it to its starting position.
- To display the variations of a signal with respect to time on an oscilloscope, a voltage/current that varies linearly with time, has to be applied to the deflection plates. This makes the signal to sweep the beam horizontally

Waveform:

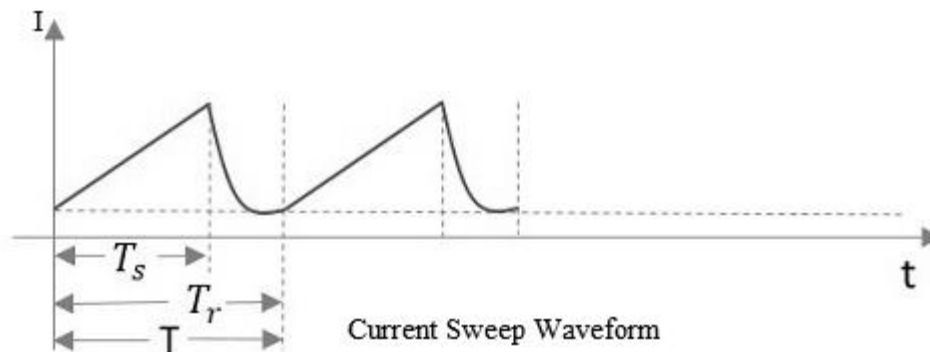

Example:

- A cathode ray tube (CRT) consists of three primary parts, the electron gun that provides a stream of accelerated electrons, the phosphor-covered screen that lights up when the electrons hit it, and the deflection plates that use magnetic or electric fields to deflect the electrons in-flight and allows them to be directed around the screen.
- It is the ability for the electron stream to be rapidly moved using the deflection plates that allow the CRT to be used to display very rapid signals.
- To display such a signal on an oscilloscope for examination, it is desirable to have the electron beam sweep across the screen so that the electron beam cycles at the same frequency as the carrier, or some multiple of that base frequency.
- This is the purpose of the current time base generator, which is attached to one of the set of deflection plates, normally the X axis, while the amplified output of the radio signal is sent to the other axis, normally Y. The result is a visual re-creation of the original waveform.

OR

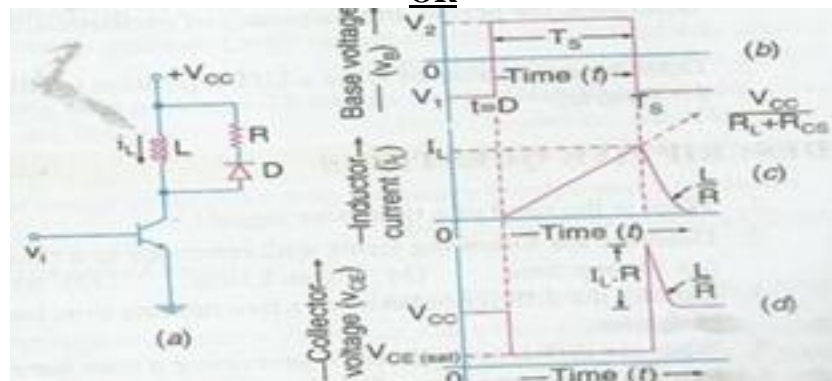


Fig: A current time base circuit.


**1M,
Example 1M**

- Above Fig. shows a simple circuit of a current time base generator.
- Here an inductor (L) in series with a transistor is connected across the V_{CC} supply.
- The transistor operates as a switch in the circuit.
- The gating waveform at the base operates between two levels. V_1 and V_2 as shown.
- The lower level (V_1) keeps the transistor in cut-off, while the upper level drives the transistor into saturation.
- When the transistor switch is turned ON, then neglecting the effect of small saturation resistance (R_{cs}), the current through and inductor (i_L) increases linearly with the time.
- The diode D does not conduct during the sweep, because it is reverse biased.

d) **Design a voltage regulator using IC LM317, draw the circuit diagram and state the output voltage equation.**

4M

Ans: **Circuit diagram:-**

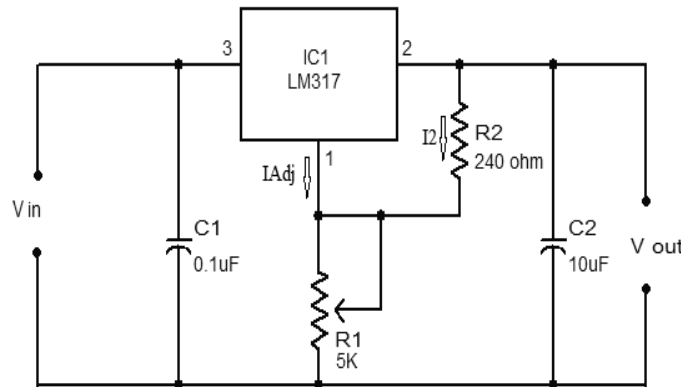

2M

- IC LM317 is adjustable three terminal positive voltage regulator, available with output voltage of 1.2v to 37v and output current from 0.1A to 18.12 A.
- Three terminals of adjustable voltage regulators are V_{in} , V_{out} , and adjustment, above fig shows connection diagram of LM 317 regulator. It requires only two external resistors to set the output voltage.
- LM 317 develops a nominal 1.25v referred to as the reference voltage. V_{ref} between output and adjustment terminals. This voltage is impressed across R_2 , since the voltage is constant; the current I_2 is also constant for given value of R_2 . In addition to I_2 , current I_{Adj} from the adjustment terminal also flows through the output resistor R_1 .
- LM317 is designed such as $I_{ADJ} = 100\mu A$ -

The output voltage V_0 is $V_0 = R_2 \cdot I_2 + R_1(I_{ADJ} + I_2)$ ---(1)

$$I_2 = \frac{V_{ref}}{R_2}$$

Substitute I_2 in equation (1)

$$V_0 = R_2 \cdot \frac{V_{ref}}{R_2} + R_1 \left(I_{ADJ} + \frac{V_{ref}}{R_2} \right)$$

$$V_0 = R_2 \cdot \frac{V_{ref}}{R_2} + R_1 \cdot I_{ADJ} + R_1 \cdot \frac{V_{ref}}{R_2}$$

$$V_0 = V_{ref} \left(1 + \frac{R_1}{R_2} \right) + R_1 \cdot I_{ADJ}$$

Where $V_{ref} = 1.25v$.

Design-1M

However the current I_{ADJ} is very small and constant. Therefore the voltage drop across R_2 due to I_{ADJ} is also very small and can be neglected.

Therefore

$$V_0 = 1.25 \left(1 + \frac{R_1}{R_2}\right)$$

The output is a function of R_1 for a given value of R_2 and can be varied by adjusting the value of R_1 . The resistor R_2 usually is 240 ohm. Normally no capacitor is needed unless the LM317 is situated far from the power supply filter capacitor.

Output equation-1M

Q.4

Attempt any THREE of the following :

12-Total Marks

a)


Draw the two stage BJT amplifier. State the formula for overall gain of this amplifier.

4M

Ans:

Diagram:

3M

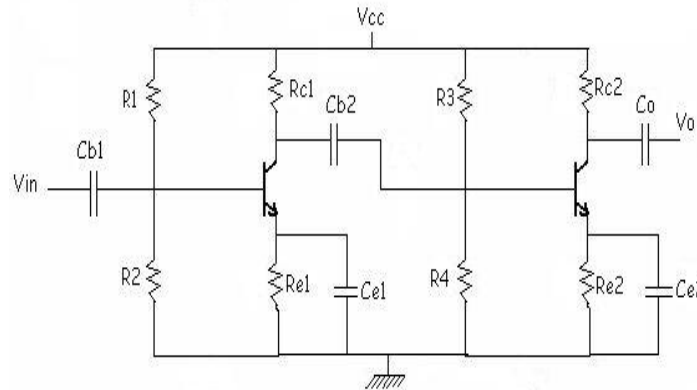

Let A_{v1} -Voltage gain of first amplifier

A_{v2} -voltage gain of second amplifier

$$\text{Overall voltage gain, } A_v = A_{v1} * A_{v2}$$

Formula 1M

b)


Draw the circuit diagram of class AB power amplifier and describe its working.

4M

Ans:

Circuit diagram:

2M

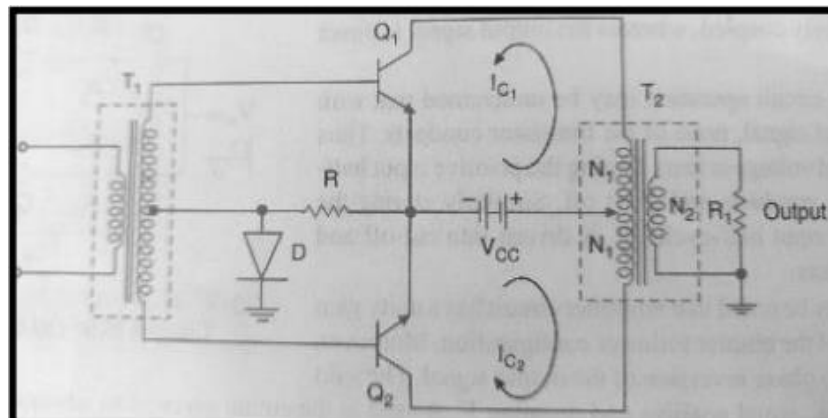

Circuit Description:

The circuit consists of two center-tapped transformers T_1 and T_2 , two identical transistors Q_1 and Q_2 , Resistor R and diode D . The DC voltage developed across the diode D is connected to the bases of both the transistors through the secondary winding

of the input transformer. This voltage acts as DC bias for the transistors because it is equal to cut-in voltage and they will conduct for complete half cycleperiod of the input to eliminate the cross-over distortion.


WORKING:

- i. When there is no a.c. input signal is applied both the transistors Q_1 & Q_2 are cut off. Hence no current is drawn from V_{CC} .
- ii. DURING POSITIVE HALF CYCLE:
 - The base of the transistor Q_1 is positive and that of Q_2 is negative.
- iii. As a result of this Q_1 conducts, while the transistor Q_2 is OFF. → DURING DURING NEGATIVE HALF CYCLE:
 - The base of the transistor Q_2 is positive and that of Q_1 is negative.
 - As a result of this Q_2 conducts, while the transistor Q_1 is OFF.
- iv. Thus at any instant any one transistor in the circuit is conducting. Then the output transformer joins these two halves & produces a full sine wave in the load resistor.

2M

OR

Circuit diagram:-

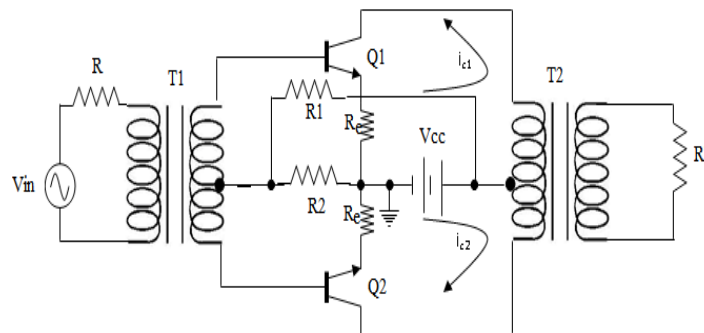

Circuit operation:-

- Resistor R_1 , R_2 are chosen to provide biasing to the transistors Q_1 , Q_2 , input transformer T_1 provides phase splitting function in which two voltages are out of phase with each other. V_{CC} is tied to the transistor collectors through the centre tapped output transformer T_2 . R_e is stabilized resistor.
- When positive half cycle of the input signal is applied, the base of Q_1 becomes positive and base of Q_2 negative. Therefore Q_1 is ON and Q_2 is OFF. As transistors Q_1 and Q_2 are biased just above cut off. Therefore as positive input cross zero, collector current i_{c1} starts flowing through Q_1 , through transformer T_2 as shown and $i_{c2} = 0$. A positive sinusoidal voltage will appear across load.
- When negative half cycle is applied across input the base of Q_1 becomes negative while the base of Q_2 is positive. Therefore Q_1 is off and Q_2 conduct, as soon as input cross zero, negative sinusoidal voltage will appear across load.

c) **With the help of neat circuit diagram, explain the operation of voltage shunt type feedback amplifier.** 4M

Ans: **Diagram:** 2M

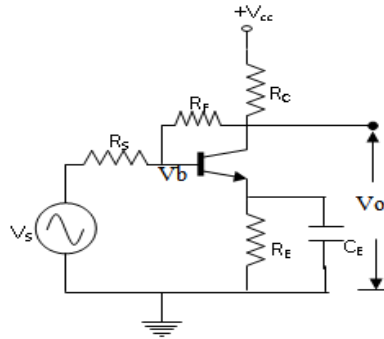


Fig. shows common emitter transistor amplifier with a feedback resistor R_F connected between its output and input terminals. This is collector to base biasing when the input signal is applied to the input then amplified output V_O is produced with 180° phase shift (out of phase with input) with the input.

Hence the feedback current is given by –

$$I_F = \frac{V_b - V_o}{R_F}$$

$$\because V_b \ll V_o$$

$$\therefore I_f = - \frac{V_o}{R_F}$$

Thus if we reduce the output voltage to zero then feedback voltage will reduce to zero, therefore it is voltage feedback. As $I_s = I_f + I_i$ it is shunt type therefore it voltage shunt negative feedback amplifier.

Explanation
2M

d) Compare between RC phase shift oscillator and crystal oscillator.

4M

Ans: (Note: Any other relevant point also can be considered.)

Sr. No.	RC phase shift oscillator	Crystal oscillator
1	This oscillator is used for low frequency range.	Quartz crystal is mainly used in radio-frequency (RF) oscillators
2	Used resistor and capacitor network to decide frequency of oscillator.	Crystal decides the frequency of oscillator.
3	RC phase shift oscillators are comparatively less stable.	crystal oscillators are highly stable
4	RC network is used as feedback network.	Crystal is connected in feedback.




Any 4 points
1M each point

e) Compare the fixed voltage regulators using 78XX and 79XX.(any four points)

4M

Ans: (Note: Any other relevant point also can be considered.)

1M each

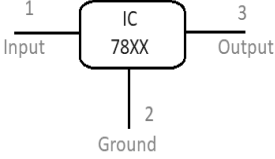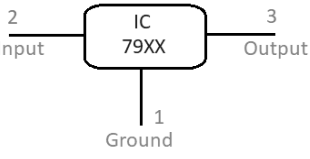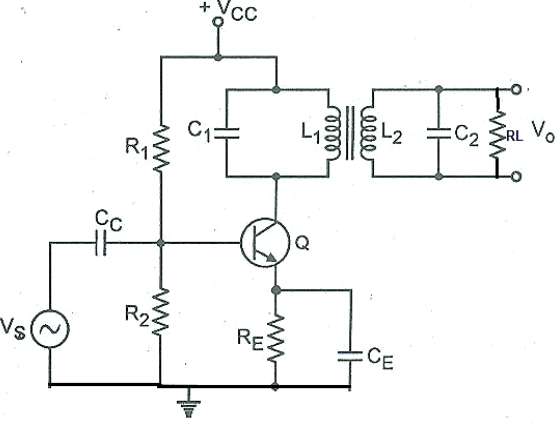		Sr. No.	78xx	79xx	point
		1	It produces positive fixed DC voltage values,	It produces negative fixed DC voltage values	
		2	IC 78xx (7805, 7806, 7808, 7812, 7815, 7818, 7824)- Positive Voltage Regulator.	IC 79xx (7905, 7906, 7908, 7912, 7915) - Negative Voltage Regulator	
		3	Output current is 1A	Output current is 1.5A	
		4	 <p>OR 1-Input 2-Ground 3-Output</p>	 <p>OR 1-Ground 2-Input 3-Output</p>	
Q.5	Attempt any TWO of the following				12 Total Marks
(a)	Describe the operation of double tuned amplifier with the help of neat circuit diagram and mention its applications.				6M
Ans:	<p>Circuit diagram:</p>  <p>Operation:</p> <ul style="list-style-type: none"> The signal to be amplified is applied at the input terminal through the coupling capacitor C_C The resonant frequency of the tuned circuit $L_1 C_1$ is made equal to that of tuned circuit $L_2 C_2$ Under these conditions the tuned circuit offers a very high impedance to the input signal. As a result of this, a large output appears across the tuned circuit $L_1 C_1$ which is inductively coupled to the $L_2 C_2$ tuned circuit. <p>Applications: (any two)</p> <p>(i) Radio and T.V broadcasting as tuning circuit.</p>				2M 2M 1M each

(ii) Wireless communication system.



(b)

Sketch the labeled diagram of class A and class B types of power amplifier. Also draw the input and output waveforms. State one application of each.

6M


Ans:

CLASS A POWER AMPLIFIER CIRCUIT DIAGRAM:

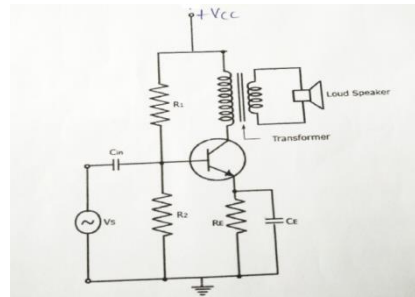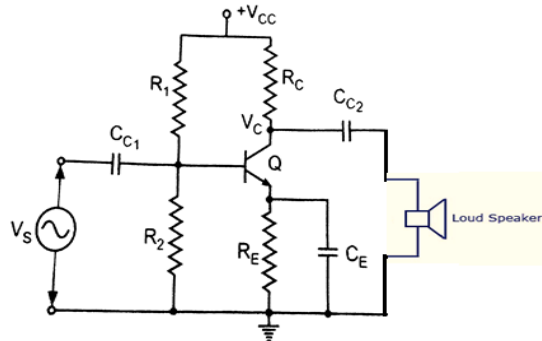

OR

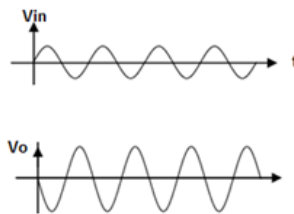CLASS A POWER AMPLIFIER I/P & O/P WAVEFORMS:



Diagram

1 1/2 M



Waveform

1M

CLASS A POWER AMPLIFIER APPLICATION:

1. High gain voltage amplifiers
2. RF & IF amplifiers in Radio & T.V.
3. Audio amplifiers

CLASS B POWER AMPLIFIER CIRCUIT DIAGRAM:

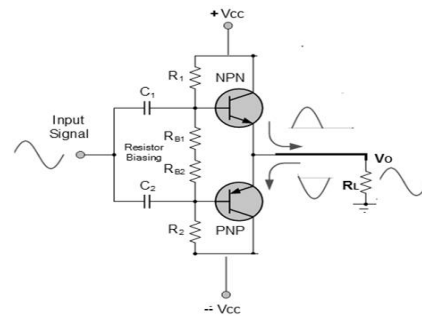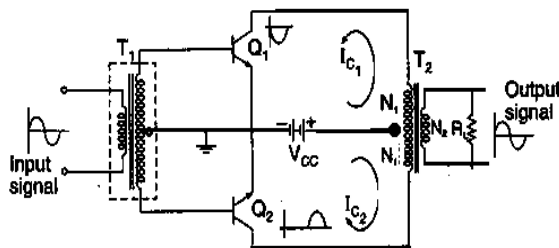


Diagram

1 1/2 M

class B push pull power amplifier complementary symmetry class B push pull power amplifier

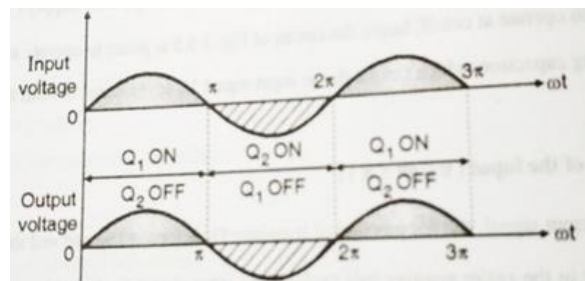CLASS B POWER AMPLIFIER I/P & O/P WAVEFORMS:



Waveform


1M

CLASS B POWER AMPLIFIER APPLICATION (Any 2):

1. Final stages of the amplifier circuits.

1/2 M

		<p>2. In public address systems (PA system)</p> <p>3. In tape recorders and music system</p> <p>4. In T.V receivers</p>	
	(c)	<p>Draw the neat labelled diagram of miller sweep generator and mention its two applications.</p>	6M
	Ans:	<p>Circuit Diagram:</p> <p>Applications (Any Two):</p> <ul style="list-style-type: none"> • In Television (TV) • In CRO • To convert step waveform into ramp waveform. 	4M 1M each
Q.6		<p>Attempt any TWO of the following:</p>	12Total Marks
	(a)	<p>For a BJT ac amplifier, with a midband voltage gain of 200, if the cutoff frequencies are $f_1=20\text{Hz}$ and $f_2=20\text{KHz}$. Draw the frequency response for amplifier. Draw the frequency response in case of mid gain of 100 and $f_1=500\text{Hz}$ to $f_2=5\text{KHz}$.</p>	6M
	Ans:	<p>(i) Frequency response for amplifier with mid-band voltage gain of 200, if the cutoff frequencies are $f_1=20\text{Hz}$ and $f_2= 20\text{KHz}$.</p> <p>(ii) Frequency response for amplifier with mid-band voltage gain of 100, if the cutoff frequencies are $f_1=500\text{Hz}$ and $f_2= 5\text{KHz}$.</p>	3M 3M

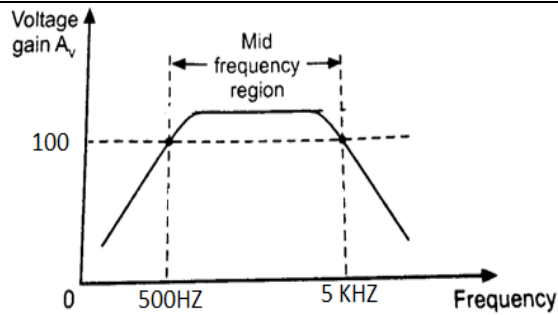


(b) Draw a class AB push pull amplifier and comment on its usefulness in the output stage as compared to other power amplifiers and the relationship between maximum transistor power dissipation w.r.t the supply voltage.

6M

Ans:

CLASS AB Push – Pull Amplifier circuit diagram:

3M

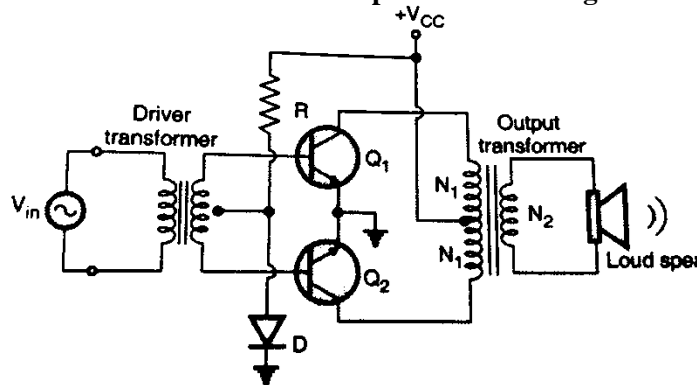

Usefulness as compared to other power amplifiers:

2M

1. Efficiency more than Class A power amplifier
2. Cross over distortion is eliminated as compared to Class B power amplifier.

Relationship between maximum transistor power dissipation w.r.t the supply voltage:

1M

$$P_D = P_{i(DC)} - P_{o(A.C.)}$$

$$= \frac{2V_{CC} * I_m}{\pi} - \frac{V_m * I_m}{2}$$

(c) Comment on the effect of negative feedback on the gain, input and output resistance of the feedback amplifiers. Describe the gain bandwidth product term used in this context and its importance.

6M

Ans:

Effect of negative feedback:

3M

1. Gain decreases with negative feedback.
2. Input resistance increases with negative feedback.
3. Output resistance decreases with negative feedback.

Explanation of significance of Gain bandwidth product

Explanation
3M

- Bandwidth measure at 3db voltage gain. As Gain and bandwidth product is always constant, and it is unity gain bandwidth.
- The gain decreases with negative feedback bandwidth increases which means it is stable output on more range of frequency.