

V2V EDTECH LLP

Online Coaching at an Affordable Price.

OUR SERVICES:

- Diploma in All Branches, All Subjects
- Degree in All Branches, All Subjects
- BSCIT/CS
- Professional Courses
- +91 93260 50669
 v2vedtech.com
- V2V EdTech LLPv2vedtech





SUMMER-18 EXAMINATION

Subject Name: Basic Electronics

Model Answer

Subject Code: 22216

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more Importance (Not applicable for subject English and Communication Skills.
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No.	Sub Q. N.			Answei	ſS	Marking Scheme
1		Attempt a	ny FIVE:			10- Total Marks
	а	State mate	erials used	d for LED's to emit different c	olour light.	2M
	Ans:	-	Sr. No. 1 2 3 4	Material used Gallium arsenide (GaAs) Gallium arsenide phospide GaAsP Gallium phospide (GaP) Gallium nitrite Ga(NO ₂) ₃	Colour of the emitted light Infrared (IR) Red or Yellow Red or Green Blue	¹ ∕₂ Mark for each correct answer
	b	Sketch the	e symbol o	of P-channel and n-channel de	epletion type MOSFET.	 2M



SUMMER-18 EXAMINATION

Subject Name: Basic Electronics

Model Answer

Ans:		1M each
	$Gate \longrightarrow Gate \longrightarrow Gate \longrightarrow Source \\ n \text{ channel} p \text{ channel}$	
C	List any two BJT biasing circuits with respect to operating point.	2M
Ans:	1) Fixed bias	Any
	2) Base biased with emitter feedback	two 1N each
	3) Collector to base bias	
	4) Voltage divider bias	
d	State different methods of biasing of FET.	2M
Ans:	1) Fixed bias	½ M
	2) Self bias	each
	3) Voltage divider bias	
	4) Source bias	
е	Sketch reverse characteristics of zener diode with proper labelling.	2M
Ans:	V _Z V _R (Volts) 0 K Breakdown I (mA)	1M diagra m 1M
	(or regulation region) M → I _{ZM} Reverse characteristic of a zener diode.	labelin



SUMMER-18 EXAMINATION

Subject Name: Basic Electronics

Model Answer

Line regulation= $\Delta V_L / \Delta V_S$		
line regulation. It is mathematically expressed as,		
The change in output voltage with respect to per unit change in input voltage is defined as		
(OR)		
Δ means "a change in"		
<i>Line regulation</i> = $\left(\frac{\Delta V_{OUT}}{\Delta V_{IN}}\right) \times 100\%$		
Formula:-		
voltage relative to the change in the input line voltage.		
over changes in the input line voltage. It is expressed as percent of change in the output		



SUMMER-18 EXAMINATION Model Answer

Subject Name: Basic Electronics


Q. No.	Sub Q. N.	Answers	Marking Scheme
2		Attempt any THREE:	12- Total Marks
	а	Describe experimental set-up for operation of P-N junction diode in forward bias. Draw its characteristics.	4M
	Ans:	Experimental set up Forward characteristics:- $R_{S} + m_{A} - I_{f} A$	2M
			1M
		 Explanation:- PN junction diode is forward biased when positive terminal of the power supply is connected to the P-type side, and the negative terminal of the power supply is connected to the N-type side. When a PN junction is forward biased, the holes are repelled from the positive terminal of the battery and are moved towards the junction. Similarly the free electrons are repelled from the negative terminal of the battery and move towards the PN junction. Because of their acquired energy (from the battery V_{FF}), some of the holes and the free electrons enter into the depletion region and recombine themselves. This reduces the potential barrier and the width of the depleting region. The width of depletion region and the barrier potential reduces with the increase in forward bias. 	
		• As a result of this, more majority carriers diffuse across the junction. Therefore, it	



SUMMER-18 EXAMINATION


Subject Name: Basic Electronics Model Answer

Subje

 



SUMMER-18 EXAMINATION

 

Dividing equation (1) by Ic

$$\frac{I_E}{I_C} = \frac{I_B}{I_C} + \frac{I_C}{I_C}$$
Therefore $\frac{1}{\alpha} = \frac{1}{\beta} + 1$
Therefore $\frac{1}{\alpha} = \frac{1+\beta}{\beta}$
 $\alpha (1+\beta) = \beta$
 $\alpha + \alpha \beta = \beta$
 $\alpha = \beta - \alpha \beta$

Therefore
$$\beta = \frac{\alpha}{1-\alpha}$$
 $\alpha = \frac{\beta}{1+\beta}$ (OR)

B

Div

 $\alpha = \beta(1 - \alpha)$

Relation Between Current Grain dan
B:
Current Grain of CB config. (d) =
$$\Delta I_{c}$$

 ΔI_{E}
Current Grain of CE config. (b) = ΔI_{c}
Current Grain of CE config. (b) = ΔI_{c}
 ΔI_{B}
We know that emitter current (IE) of a
transister is the sum of it's base current
(IB) and collector current (IC) i'e,
 $I_{E} = I_{c} + I_{B}$
 $\Delta I_{E} = \Delta I_{c} + \Delta I_{B}$

$$\begin{array}{c} \text{in } eq^{\text{W}} (2) \\ = & \underline{AIc} \\ \Delta I \in -\Delta Ic \\ \hline \Delta I \in -\Delta Ic \\ \hline \Delta I \in -\Delta Ic \\ \hline \Delta I \in \\ AI \in \\ \hline \Delta I E \\ \hline \Delta I \in \\ \hline \Delta I E \\ \hline \hline \Box I E \\ \hline \hline \hline I E \\ \hline \hline \Box I E \\ \hline \hline I E \\ \hline I E \\ \hline \hline I E \\ \hline$$

A=B

ATE

· AIC

[since $\alpha = \frac{I_C}{I_E}$, $\beta = \frac{I_C}{I_B}$]

Subject Code: 22216

2M



SUMMER- 18 EXAMINATION

Subject Name: Basic Electronics

Model Answer

с	Explain basic block diagram of regulated DC power supply, draw its input and output	4M
C	waveforms.	
Ans:	Block diagram of regulated DC power supply:-	2M
	Vm ^{sinot} Vm ^{sinot} To To AC line Trans- former Rectifier Filter Regulator Vout Load	
	Explanation	
	1)Transformer	
	2) Rectifier	
	3) Filter	
	4) Voltage regulator.	
	1. Transformer:- The AC main voltage is applied to a step down transformer. It reduces	
	the amplitude of ac voltage to the desired level and applies it to a rectifier.	
	2. Rectifier: The rectifier is usually a centre tapped or bridge type full wave rectifier. It	2M f expl
	converts the ac voltage into a pulsating dc voltage.	ion
	3. Filter: The pulsating dc (or rectified ac) voltage contains large ripple. This voltage is	
	applied to the filter circuit and it removes the ripple. The function of a filter is to	
	remove the ripples to provide pure DC voltage at its output.	
	The DC output voltage thus obtained will change with the changes in load current, input voltage, etc. So it is unregulated DC voltage.	
	4. Voltage Regulator :- The unregulated DC voltage is applied to a voltage regulator. Output of the regulator circuit will be constant voltage under all operating circumstances.	



SUMMER-18 EXAMINATION Model Answer

Subject Name: Basic Electronics

d	Exp	plain the need of stabilization of Q point.	4M
Ans:	•	Bias stabilization is a process of stabilizing the position of operating point "Q"	4M
	•	The stabilization of Q-point is necessary to maintain the Q-point at the centre of load	
		line because the bias point (Q-point) changes its position on the load line due to the	
		factors such as temperature or device to device variations.	
	•	If the Q-point gets shifted towards saturation or cut off regions, then amplified output	
		waveform is distorted. In order to avoid such distortion it is necessary to stabilize the	
		Q-point at the centre of the load line.	
	•	So we need to design a biasing circuit which will keep the position of Q-point stable on	
		the load line.	



SUMMER-18 EXAMINATION Model Answer

Subject Name: Basic Electronics

Q. No.	Sub Q. N.	Answers	Marking Scheme
3		Attempt any four:	16- Total Marks
	а	Describe circuit diagram of bridge rectifier, draw its input and output waveforms.	4M
	Ans:	Circuit diagram:	Circuit diagram2M
			Explanation 1M
		$ \begin{array}{c} \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\$	Waveform 1M
		When input AC signal is applied across the bridge rectifier, during the positive half cycle	
		diodes D_1 and D_2 are forward biased and conduct while the diodes D_3 and D_4 are reverse	
		biased and current flows through the load from point A-D ₁ -load-D ₂ -point B.	
		During the negative half cycle diodes D ₃ and D ₄ are forward biased and conduct while	
		diodes D_1 and D_2 are reverse biased and current flow through the load from point B-D ₃ -	
		load-D₄-point A.	
		As the current flowing through the load is unidirectional, the voltage developed across	
		the load is also unidirectional as shown in the waveform.	
		Vin \uparrow Voltage across RL Vout \uparrow D1D2 D3D4 D1D2 D3D4 t	
	I		Page 9 / 25



SUMMER-18 EXAMINATION Model Answer

Subject Name: Basic Electronics


b	Evaluin the working of positive element with proper sizewit diagram and draw the	4M	
D	Explain the working of positive clamper with proper circuit diagram and draw the waveforms at input & output of clamper.	4111	
Ans:	Positive clamper circuit:	Circuit diagram	
	$v_m \rightarrow v_m \leftarrow \mathbf{A}$	Explana 1M Wavefo	
	Fig. 2 Positive Clamper		
	• The circuit will be called a positive clamper, when the signal is pushed upward by the circuit.		
	• During the positive half cycle, the diode is reverse biased.		
	• During the negative half cycle, it is forward biased and current flows through it. It charges the capacitor to the negative peak voltage -V _m		
	 Once the capacitor is fully charged to -V_m, cannot discharge because the diode cannot conduct in the reverse direction. 		
	• Therefore the capacitor acts as a battery with e.m.f equal to -V _m .		
	• This voltage gets added to the input signal, $V_m.sin\omega t$.		
	• Therefore the output voltage is equal to , $v_0 = V_m . \sin \omega t + V_m$		
	• Thus a d.c voltage equal to V _m is added to input signal. It causes the waveform to clamp positively at 0 V.		
С	A JFET has I_{Dss} = 10 mA, V_P = -5 volts, gmo = 2 ms. Calculate the trans-conductance and	4M	
	drain current of the JFET for V_{Gs} = -2.5 volts.		
Ans:	The expression for drain current ID, in the saturation region is,		
	$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$		
		Formula	



SUMMER-18 EXAMINATION

Subject Name: Basic Electronics

Model Answer

 




SUMMER-18 EXAMINATION

Subject Name: Basic Electronics

Model Answer

 



SUMMER-18 EXAMINATION Model Answer

Subject Name: Basic Electronics

Q. No.	Sub Q. N.	Answers				Markin g Scheme
4		Attempt any THREE:				12- Total Marks
	а	(ii) Rectification ef	de used in circui	t.	ave rectifiers :	4M
	Ans:	(iv) Ripple factor				1M each
		Parameters	Half wave	Full wave Center-tapped	Bridge	
		No of diodes	1	2	4	
		Rectification Efficiency TUF	40.6% 0.287	81.2% 0.693	81.2% 0.812	
		Ripple factor	1.21	0.482	0.482	4M
	b	Explain the operation of NPN transistor in the active region.				
	Ans:					Diagram- 2M
			V _{BE} +	+ v _{ce}		Operatio n-2M
		Operation of NPN transistor in Active region is one in which bas		is forward biased and	base collector junction will	Note: Any other configur ation can be
			-		-	consider



SUMMER-18 EXAMINATION Model Answer

Subject Name: Basic Electronics


	be reverse biased in a transistor.	ed
	Due to forward bias at base emitter junction, the barrier potential is reduced and results in electron flow from emitter to base or current I_E .	
	Some of the electrons entering base region will combine with holes in the base region and result in base current I_B .	
	Remaining large number of electrons will pass to the collector circuit and represent the collector current $I_{c\cdot}$	
	In the active region, the collector current increases slightly(nearly constant) as collector-emitter voltage V_{CE} increases. The value of the collector current I_C increases with the increase in I_B .	
	In the active region $I_C = \beta I_{B.}$	
С	Draw the input and output characteristics of CE configuration with proper labelling of various regions.	4M
Ans:		2M each



SUMMER-18 EXAMINATION

Subject Name: Basic Electronics

Model Answer

 



SUMMER-18 EXAMINATION

Subject Name: Basic Electronics

Model Answer


Subject Code: 22216

will reduce the number of free electrons in the channel for conduction. So drain current reduces. The value of V_{GS} at which drain current is nearly equal to zero is called cut off voltage.


When gate is positive with respect to source, then positive V_{GS} draws additional electrons from the P type substrate. Thus drain current (I_D) increases as increase in positive V_{GS} .

OR

Enhancement – Type MOSFET:-

 

Circuit Operation:

 

In fig. both V_{GS} & V_{DS} have been set at positive with respect to the source. The positive potential at the gate will attract the electrons from the P substrate & accumulate in the region near to the surface of SiO_2 layer. The SiO_2 layer & its insulating qualities will prevent the negative carriers (i.e. electrons) from being absorbed at the gate.


As V_{GS} increases, the concentration of electrons near the SiO₂ surface increases & there is formation of channel & the current starts following through the circuit for further applied voltage.



SUMMER-18 EXAMINATION

Subject Name: Basic Electronics

Model Answer

 



SUMMER-18 EXAMINATION Model Answer

Subject Name: Basic Electronics

Q. No.	Sub Q. N.	Answers	Marking Scheme
5		Attempt any TWO:	12- Total Marks
	а	Explain drain characteristics of JFET with ohmic region, saturation region, cut-off region and break down region.	6M
	Ans:	The drain characteristics of JFET can be explained as follows: Ohmic Region:	3 Marks for characteristics
		This region is represented by curve OA in the figure. In this region, the drain current increases linearly with the increase in drain-to-source voltage, obeying Ohm's law. The linear increase in drain current is due to the fact that N-type semiconductor bar acts like a simple resistor.	
		Curve AB: In this region, the drain current increases at the reverse square law rate with the increase in drain-to-source voltage. It means that drain current increases slowly as compared to that in ohmic region. It is because of the fact, that with the increase in drain-to-source voltage, the drain current increases. This in turn increases the reverse	1 Mark for Each region



SUMMER-18 EXAMINATION Model Answer

Subject Name: Basic Electronics


Ans:	Circuit diagram of full wave rectifier connected with π filter: 230 V A.C. Input and Output waveforms of full wave rectifier connected with π filter	3Marks for Circuit diagram
b	Draw circuit diagram and input and output waveforms of full wave rectifier connected with π filter.	6M
	This region is shown by the curve CD. In this region, the drain current increases rapidly as the drain-to-source voltage are increased. It happens because of the breakdown of gate-to-source junction due to avalanche effect. The drain-to-source voltage corresponding to point C is called breakdown voltage.	
	The above relation is known as Shockley's equation. The pinch off region is the normal operating region of JFET, when used as an amplifier. Breakdown region:	
	$I_D = I_{DSS} (1 - \frac{V_{GS}}{V_p})^2$	
	This region is shown by the curve BC. It is also called saturation region or constant current region. Here the drain current remains constant at its maximum value (i.e. I _{DSS}). The drain, current in the pinch off region, depends upon the gate-to-source voltage and is given by the relation	
	Pinch off region:	
	bias voltage across the gate-source junction. As a result of this, the depletion region grows in size, thereby reducing the effective width of channel. At the drain-to-source voltage, corresponding to point B, the channel width is reduced to a minimum value and is known as pinch off. The drain-to-source voltage, at which the channel pinch-off occurs is known as pinch-off voltage (V_p)	



SUMMER-18 EXAMINATION

Subject Name: Basic Electronics

Model Answer

 



SUMMER- 18 EXAMINATION

Subject Name: Basic Electronics

Model Answer


		It indicates that forward current is very small for voltages below knee (cut-in) voltage and large for voltages above knee voltage. Reverse characteristics : Zener diode is silicon p-n junction device which differs from a rectifier diode, in the sense, that it is operated in the reverse breakdown region. When the reverse voltage across a diode is increased a critical voltage called breakdown voltage, the reverse current increases sharply as shown in the curve KM. This is an indication that the breakdown has occurred. This breakdown voltage is called as Zener breakdown voltage or Zener voltage and it is denoted by V _z . The breakdown voltage of Zener diode is set by carefully controlling the doping level during manufacture. After breakdown has occurred, the voltage across Zener diode remains constant equal to V _z . Any increase in the source voltage will result in the increase in reverse Zener current.	4 Marks for description
Q. No	Sub Q. N.	Answers	Marking Scheme
6		Attempt any TWO:	12- Total Marks
	а	Show constructional details of LED. Give any two applications of LED.	6M
	Ans:	Constructional details of LED: A pn junction diode, which emits light when forward biased, is known as a light emitting	2 Marks for
		diode (LED). This emitted light may be visible or invisible. The amount of light output is directly proportional to the forward current. Thus higher the forward current, higher is the light output.	Construction
		Here, an N-type layer is grown on P-type substrate by a diffusion process. Then a thin P- type layer is grown on N-type layer. It has two electrodes namely Anode and Cathode. The light energy is released at the junction, when the recombination of electrons with the holes takes place. After passing through the P-region, the light is emitted through the window provided at the top of the surface.	



SUMMER-18 EXAMINATION

Subject Name: Basic Electronics

Model Answer

 




SUMMER-18 EXAMINATION

Subject Name: Basic Electronics

Model Answer

 



SUMMER-18 EXAMINATION Model Answer

Subject Name: Basic Electronics

	 dc voltage to pass through .Hence it is also known as blocking capacitors. The capacitor C_E works as a bypass capacitor. It bypasses all the AC currents from the emitter to the ground and avoids the negative current feedback. It increases the output AC voltage. The resistance R_L represents the resistance of whatever is connected at the output. It may be load resistance or input resistance of the next stage. 				
С	(i) C (ii) F (iii) A	tiate clipper and clam Components used in ci Cunction Application Configuration	nper with following points: rcuit.		6M
Ans:	Sr.No. 1 2 3	Parameter Components used in circuit Function Application	Clipper Diode, resistor To remove a part of input signal voltage above or below a certain level. • Digital computers,	Clamper Diode, resistor, capacitor To add a DC shift to the input signal • Used in Television	2 Marks for Component used in circuit
			 radars, radio and television receivers, to limit the amplitude of the input signal voltages required in several applications. 	 receivers to restore the original dc reference signal to the video signal, voltage multipliers. 	1 Mark for Function 1 Mark for Application 2 Mark for Configuration



SUMMER-18 EXAMINATION

Subject Name: Basic Electronics

Model Answer

4	Configuration			
Note: A	ny related configuratio	on can be considered for clip	per and clamper	



V2V EDTECH LLP

Online Coaching at an Affordable Price.

OUR SERVICES:

- Diploma in All Branches, All Subjects
- Degree in All Branches, All Subjects
- BSCIT/CS
- Professional Courses
- +91 93260 50669
 v2vedtech.com
- V2V EdTech LLPv2vedtech





MODEL ANSWER

WINTER-18 EXAMINATION

Subject Title: Basic Electronics (BEL)

Subject Code:

22216

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more Importance (Not applicable for subject English and Communication Skills.
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for anyequivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No.	Sub Q.N.	Answer	Marking Scheme
Q.1		Attempt any FIVE :	10-Total Marks
	a)	Draw the symbol of photodiode.	2 M
	Ans:	Anode Cathode	Correct symbol -2M
	b)	Define Transistor. State its type.	2M
	Ans:	Transistors are active electronic components made of semiconducting materials, which can amplify the electric signals by the application of a small input signal.Types of transistors:1. Unipolar Junction Transistors	Definition - 1M; Types - 1M
		2. Bipolar Junction Transistors	ijpeo ini
	c)	Define load and line regulation.	2M
	Ans:	Load regulation is the ability of the power supply to maintain its specified output voltage given changes in the load. Line regulation is the ability of the power supply to maintain its specified output voltage over changes in the input line voltage.	Each definition - 1M



d)	State application of FET.	2M
Ans:	(NOTE : Any other relevant Application mark shall be given)Applications of FET :i. As input amplifiers in oscilloscopes, electronic voltmeters and other measuring and testing equipment because high input impedance reduces loading effect to the minimum.ii. Constant current source.They are used to build RF amplifiers in FM tuners and other communication circuits.Because of low noise.iv. FETs are used in mixer circuits of FM and TV receivers as it reduces inter modulation distortion.v. Used as Analogue switch.vi. As a Voltage Variable Resistor (VVR) in operational amplifiers.	Any two applications (1M each)
e)	Sketch energy band diagram of semiconductor.	2M
Ans:	Energy band diagram for N type semiconductor: Conduction energy band Jackborn Fermi lavel - donor donor material Valence Energy Band Energy band diagram for P type semiconductor: Conduction Band Fermi lavel - Fermi lavel - Fermi lavel	Any one correct diagram - 2M
	Valence Band Increased holes due to acceptoral material	



	f)	State the need of DC regula	ted power supply.		2M
	Ans:	Need of DC regulated powe 1. To convert unregulated AC 2. To convert fluctuating mai		nt DC.	Any one relevant need - 2M
	g)	Name the components of fo	llowing symbol:		2M
	Ans:	(i) N-channel Enhancement t (ii) N-channel Depletion type			Each correct answer -1M
Q. 2		Attempt any THREE of the	following :		12-Total Marks
	a)	Compare PN junction diod	e & Zener diode. (four points	5).	4 M
	Ans:	Parameter Symbol	PN junction diode	Zener diode	Each point - 1M
		Direction of Conduction	Conducts only in one direction	Conducts in both directions	
		Reverse breakdown	It has no sharp reverse breakdown	It has quite sharp reverse breakdown	
		Application Resistance in reverse biased condition	Used in rectification Very high	Used in regulation Very small	
		Characteristics	reverse voltage	Zener Diode I-V Characteristics Curve	




b)	Explain with a neat circuit diagram of voltage divider bias method for biasing a	4 M
Ans:	transistor. The voltage divider is formed using external resistors R ₁ and R ₂ . The voltage across R ₂ forward biases the emitter junction. By proper selection of resistors R ₁ and R ₂ , the operating point of the transistor can be made independent of β . In this circuit, the voltage divider holds the base voltage fixed independent of base current provided the divider current is large compared to the base current. The voltage at transistor base, V _B = V _{CC} X $\frac{R_2}{R_1 + R_2}$ Neglecting V _B , The emitter current = I _E = $\frac{V_E}{R_E}$ $V_{CE} = V_{CC} - I_C \cdot R_C - I_E \cdot R_E$	Explanation - 2M Diagram - 2M
c)	Draw the block diagram of DC power supply. Explain the function of each block.	4M
Ans:	Image: Second state of the second s	Diagram - 2M Functions - 2M
d)	Explain the concept of DC load line and oprating point.	4M
Ans:	$\begin{array}{l} \underline{DC \ load \ line}: \ The \ straight \ line \ drawn \ on \ the \ characteristics \ of \ a \ BJT \ amplifier \ which \ give \ the \ DC \ values \ of \ collector \ current \ I_C \ and \ collector \ to \ emitter \ voltage \ V_{CE} \ corresponding \ to \ zero \ signal \ i.e. \ DC \ conditions \ is \ called \ DC \ load \ line. \ To \ plot \ I_{C(MAX)}, \ V_{CE} \ (MAX) \ on \ output \ characteristics: \ Get \ V_{CE} \ (MAX) \ by \ putting \ I_{c=0} \ V_{CE} \ (MAX) \ by \ putting \ I_{c=0} \ V_{CE} \ (MAX) \ by \ putting \ V_{CE} \ since \ I_c = 0 \ Get \ I_{C(MAX)} \ by \ putting \ V_{CE} = 0 \ I_{C(MAX)} \ by \ putting \ V_{CE} = 0 \ I_{C(MAX)} \ by \ putting \ V_{CE} = 0 \ I_{C(MAX)} \ by \ putting \ V_{CE} = 0 \ I_{C(MAX)} \ by \ putting \ V_{CE} = 0 \ I_{C(MAX)} \ by \ putting \ V_{CE} = 0 \ I_{C(MAX)} \ by \ putting \ V_{CE} = 0 \ I_{C(MAX)} \ by \ putting \ V_{CE} = 0 \ I_{C(MAX)} \ by \ putting \ V_{CE} = 0 \ I_{C(MAX)} \ by \ putting \ V_{CE} = 0 \ I_{C(MAX)} \ by \ putting \ V_{CE} = 0 \ I_{C(MAX)} \ by \ putting \ V_{CE} = 0 \ I_{C(MAX)} \ by \ putting \ V_{CE} = 0 \ I_{C(MAX)} \ by \ b$	1M 2M

		MAHARASHTRASTATE BOARD OF TECHNICAL EDUCATION (Autonomous) (ISO/IEC - 27001 - 2013 Certified)	
		Saturation When $V_{CE} = 0$ $I_C = \frac{V_{CC}}{R_L}$ $I_C = \frac{V_{CC}}{R_L}$ $V_{CC} = V_{C$	1M
Q. 3		Attempt any THREE of the following:	12-Total Marks
	a) Ans:	An AC supply of 230 V is applied to HWR through a transformer with turns ratio 10:1. Find Average DC output, Voltage current and PIV of diode, RMS value of voltage and current. Vrms=230V, np/ns=10/1 Max primary voltage is $Vp=\sqrt{2}* Vrms$ $=\sqrt{2}* 230$ =325.22Volt The max secondary voltage is Vm=ns/np*Vp= =1/10*325.22 =32.52V V average=Vdc=Vm/II	4M Vdc =
		=32.5/3.14 =10.35V PIV=Vm= 32.52V Vrms=Vm/2 =32.52/2 =16.25V Idc=Im/ π Irms= Im/2	1 Mark PIV = 1 Mark
		Assume $R_{L=10K\Omega}$ - (Note - Students may assume any value and attempt to solve, can be considered)	



	$Im=Vm/R_{L}$ =32.52/10 =3.25mA $Idc=Im/\pi$ =3.25*10 =1.03 mA Irms=Im/2 =3.25*1 =1.62 m	h^{-3}/π A $(0^{-3}/2)$		Idc = 1 Mark Irms = 1mark
b)	State the va (i) (iii	Ripple factore (ii)	s with reference to full wave rectifier:) Efficiency v) P/V	4M
Ans: c)	(i) (ii) (iii) (iv Compare E	Efficiency - 81.2%) TUF -69.3 or 81.2		1 mark each parameter
Ans:				4 M
	<u>Sr. No.</u> 1	E MOSFET Insulating oxide layer is present between gate and substrate channel is absent. At the operation induced channel get created.	DMOSFET An insulating oxide layer is present between G & channel n or p-type channel is present.	Any 4 points – 1mark each
		For n- channel EMOSFET	For an n-channel DMOSFET, the V_{GS}	
	2.	V_{GS} will be only positive.	can be negative for depletion mode & positive for Enhancement mode	
	3		•	



 




		$Is=Iz+I_{L}$ $Iz=Is- I_{L}$ =0.02 - 0.0008 = 0.0192A iv)Power dissipat =V _L * I _L = 8* 0.0008 = 0.0064 =6.4mW					Power dissipation = 1mark
Q. 4	a)			ving: 1 the basis of usef	ulness in reduci	ng ripple or	12-Total Marks 4M
	Ans:	sunavinty for ne	avy / light luau.				ripple or
	Ans.	Parameters	L filter	C filter	LC filter	п filter	suitability
		Ripple	MORE	LESS	LOW	LOWEST	for heavy /
		Suitability for	HEAVY	LIGHT LOAD	HEAVY	LOW LOAD	light load = 1
		heavy / light	LOAD	LIGHT LOND	LOAD	CURRENT	mark each
		load.	Lond		CURRENT	CONTRACT	point
	b)		ating principle o	f PNP transistor.			4M
	Ans:						Diagram – 1
							mark
		in the second	Р	N	Р		Explanation
		analas delet			0 0 0 0		= 3marks
		E	1000		0000	LC	
			000	0 0 0 0	0000		
			000	0 0 0 0	0 0 0 0		
		+ ''E	L				
		+		T		Τ.	
		-		AOB		Ť	
				IBI			
				ode, i.e. the emitte			
						ased, the emitter –	
				ed only if the emit			
			r potential which i	s 0.7 volts for silic	on and 0.3 volts	for germanium	
		transistors.					
		The forward biase	ed on the emitter h	ase (E-B) junction	causes maiority	carriers i e holes	
				towards the N type			




d)	Compare BJT & JFET with reference to following point: i) Symbol ii) Transfer characteristics	4 M
	$Collector-to-emitter Vccvoltage (V_{cc})$ By KVL VcE= Vcc - Ic.Rc For point on X axis—Ic=0 VcE= Vcc=10V For point on Y AXIS VCE=0 Ic=Vcc/Rc = 10/2000 = 0.005 =5mA	Ic = 2mark V _{CE} = 2marks
Ans:	V _{cc} Saturation point (or upper end) Active region Cut-off point (or lower end) V _{cc}	
	$R_{\rm B} = 290 \ \mathrm{k}\Omega$	
c)	current due to thermally generated carriers. This current component is called reverse saturation current (I_{CO}) and is quite small. In this way, almost entire emitter current flows in the collector circuit, it is clear that the emitter current is the sum of the base current and collector current i.e. $I_E = I_B + I_C$ Find the Q point values for the following circuit, Assume $V_{BE} = 0.7 V \& \beta = 60$.	4M



 




 




		(150/1EC - 2/001 - 2013 Certified)	
		current I _z increases. Thus the value of input current and voltage drop across series resistance is kept constant. Hence the load voltage remains constant.	
		CONDITION 2. WHEN LOAD RESISTANCE IS REDUCED	
		When load resistance is decreased, the load current increases. This leads to decrease in I _Z . Because of this the input current and the voltage drop across series resistance remains constant. Hence the load voltage is also kept constant.	
Q.5		Attempt any TWO of the following :	12-Total Marks
	a)	With neat circuit diagram and mathematical expressions, explain the self-biasing used in F.E.T.	6M
	Ans:	 I. SELF BIASING In this circuit there is only one drain supply and no gate supply. The gate terminal is connected through resistor R_G to the ground. (NOTE: In JFET input PN junction between gate & source is always reverse bias, due to this input resistance of JFET is very high. Due to this input gate current I_G = zero. Hence if resistor R_G is connected in series with gate terminal, voltage drop across R_G is zero as V_{RG} = I_G R_G = 0 V_G = I_G R_G = 0 V_G = I_G R_G = 0 V_G = V_G - V_S = -V_S APPLY KVL TO INPUT LOOP V_{GS} = 1_DR_S I_D = I_DSs {1^{V_{GS}}/_{V_P}² Shockley's equation APPLY KVL TO OUTPUT LOOP V_{DD} - I_DR_D - I_DR_S = 0 V_{DSQ} = V_{DD} - I_DR_D - I_DR_S 	Circuit Digram:3M Explanation: 1M Mathematic al expression:2 M



 



 



•	Efficiency: LEDs emit more lumens per watt than incandescent light bulbs. Color: LEDs can emit light of an intended color. This is more efficient and can	Advanta
•	lower initial costs. Size: LEDs can be very small (smaller than 2 mm ²) and are easily attached to printed circuit boards.	1M (2Points
•	On/Off time: LEDs light up very quickly. LEDs used in communications devices can have even faster response times.	
•	Dimming: LEDs can very easily be dimmed either by pulse-width modulation or lowering the forward current.	
•	Cool light: In contrast to most light sources, LEDs radiate very little heat. Slow failure: LEDs mostly fail by dimming over time, rather than the abrupt failure of incandescent bulbs.	
•	Lifetime: LEDs can have a relatively long useful life. product. Shock resistance: LEDs, being solid-state components, are difficult to damage with external shock, unlike fluorescent and incandescent bulbs, which are fragile. Focus: The solid package of the LED can be designed to focus its light.	
	Disadvantages (Any Two Points):	
•	 High initial price: LEDs are currently more expensive (price per lumen) on an initial capital cost basis, than most conventional lighting technologies. Temperature dependence: LED performance largely depends on the ambient temperature of the operating environment – or "thermal management" properties. 	Disadva
•	Voltage sensitivity: LEDs must be supplied with the voltage above the threshold and a current below the rating. Current and lifetime change greatly with a small change in applied voltage.	es: 1M (2Points
•	Light quality: Most cool-white LEDs have spectra that differ significantly from a black body radiator like the sun or an incandescent light.	
•	Area light source: Single LEDs do not approximate a point source of light giving a spherical light distribution.Efficiency droop: The efficiency of LEDs decreases as the electric current	
•	increases. Heating also increases with higher currents which compromise the lifetime of the LED.	
•	Impact on insects: LEDs are much more attractive to insects. Use in winter conditions: Since they do not give off much heat in comparison to traditional electrical lights, LED lights used for traffic control can have snow obscuring them, leading to accidents.	
A	pplications of LED (Any Two Points): <u>:</u>	
•	As a power indicator.	
•	In seven segment display.	Applica
	In the opto-couplers.	1M
•	In the infrared remote controls.	(2Point



	v circuit and describe working of full wave rectifier using center tapped sformer with waveforms.	6M
	wave Rectifier with Center tapped transformer(FWR):	
•	In full wave rectification, the rectifier conducts in both the cycles as two diodes	Circuit
	are connected.	Diagram:2
Circui	iit diagram:	М
•	hit diagram: $ \begin{array}{c} \begin{array}{c} \begin{array}{c} \begin{array}{c} \begin{array}{c} \begin{array}{c} \begin{array}{c} \begin{array}{c}$	Diagram:2 M Description 2M



	v_{s} V_{m} $\frac{1}{\pi/2}$	Waveforms: 2M
c)	 i) In CE configuration if β = 99 leakage current I_{CEO} = 50 μA. If base current is 0.5 mA. Determine I_C and I_E. ii) Derive relation between α & β. 	6M
Ans:	i) Given: $\beta = 99$ $I_{CEO} = 50 \ \mu A$, $I_B = 0.5 \ mA, = 500 \ \mu A$ To Find: $I_C \& I_E$ Solution: $I_C = \beta * I_B + I_{CEO}$ Therefore, $I_C = 99 \ x \ 500 \ \mu A + 50 \ \mu A$ $I_C = 49550 \ \mu A$ Therefore, $IC = 49.55 \ m A$ $I_E = I_C + I_B$ $I_E = 49.55 \ m A + 0.5 \ m A$ $I_E = 50.05 \ m A$ ii) Relation between $a \& \beta$: We know that; $I_E = I_B + I_C(i)$ Dividing equation (i) by I_C . $I_E / I_C = I_B / I_C + I_C / I_C$ Therefore $1/\alpha = 1/\beta + 1$ (Since $\alpha = I_C / I_E$, $\beta = I_C/I_B$	To find Ic and IE = 1/5marks each Derive relation between α & β = 3marks



Therefore $1/\alpha = \frac{1+\beta}{\beta}$ Therefore $\alpha = \frac{\beta}{1+\beta}$ $\alpha(1+\beta) = \beta$ $\alpha + \alpha\beta = \beta$ Therefore $\alpha = \beta - \alpha\beta$ Therefore $\alpha = \beta (1 - \alpha)$ Therefore $\beta = \frac{\alpha}{1-\alpha}$



V2V EDTECH LLP

Online Coaching at an Affordable Price.

OUR SERVICES:

- Diploma in All Branches, All Subjects
- Degree in All Branches, All Subjects
- BSCIT/CS
- Professional Courses
- +91 93260 50669
 v2vedtech.com
- V2V EdTech LLPv2vedtech



tified)

Subject Name: Basic Electronics

MAHARASHT (Autonomous) (ISO/IEC - 2700

WINTER-19 EXAMINATION

Subject Code:

22216

Model Answer

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in themodel answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may tryto assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given moreImportance (Not applicable for subject English and Communication Skills.
- 4) While assessing figures, examiner may give credit for principal components indicated in thefigure. The figures drawn by candidate and model answer may vary. The examiner may give credit for anyequivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constantvalues may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No.	Sub Q. N.	Answers	Marking Scheme
1	(A)	Attempt any FIVE of the following:	10- Total Marks
	(a)	Define : Intrinsic semiconductor and Extrinsic semiconductor.	2M
	Ans:	Intrinsic – Semiconductor in pure form is called as intrinsic semiconductor. Extrinsic – Semiconductor with added impurity is called as extrinsic semiconductor.	Each definitio n : 1M
	(b)	State any two applications of FET.	2M
	Ans:	 Applications of FET : As input amplifiers in oscilloscopes, electronic voltmeters and other measuring and testing equipment because high input impedance reduces loading effect to the minimum. As Constant current source. They are used to build RF amplifiers in FM tuners and other communication circuits. Because of low noise. 	Any two : 2M

WINTER-19 EXAMINATION

Subject Code:

22216


	 FETs are used in mixer circuits of FM and TV receivers as it reduces inter modulation distortion. Used as Analog switch. As a Voltage Variable Resistor (VVR) in operational amplifiers. 	
(c)	Draw symbol of NPN and PNP transistor.	2M
Ans:	B E C B C C C C C NPN PNP	Each symbol 1M
(d)	Sketch the drain characteristics of N-channel MOSFET.	2M

WINTER-19 EXAMINATION

Subject Code:

```
22216
```

Model Answer

 

WINTER-19 EXAMINATION

Subject Code:

22216

Model Answer

	Ans:	Fig. No. 1 Fig. No. 2 Fig no. 1 : LED Fig no. 2 : Zener Diode	Each symbol : 1M
Q. No.	Sub Q. N.	Answers	Marking Scheme
2		Attempt any THREE of the following:	12- Total Marks
	1		

				IVICI INS
a)	Compare P-N junction of	liode and zener diode on follow	ing parameters:	4M
	(i) Symbol (ii) Doping level			
	(iii) Breakdown (iv) Applications	Voltage		
Ans:	Parameter	PN junction diode	Zener diode	Four
	Symbol			points : 4M
	Doping level	Low	High	



WINTER-19 EXAMINATION

Subject Code:

22216


	Breakdown voltage	It has no sharp reverse breakdown	It has quite sharp reverse breakdown	
	Applications	Used in rectification	Voltage stabilizer, motor protection and wave shaping	
b)	Sketch input and output c characteristics.	haracteristics of CE configuratio	n. Label various regions on	4M
Ans:		V V _{CE} = 20 V		Each charact ristic : 2M

WINTER-19 EXAMINATION

Subject Code:

22216

Model Answer

 

WINTER-19 EXAMINATION

Subject Code:

22216

Model Answer

	constant. As both of them are maintained equal, any change in the input supply is	
	indicated by the change in emitter base voltage V_{BE} .	
	 Hence the output voltage Vo can be understood as 	
	$V_{O}=V_{Z}-V_{BF}$	
	$v_{O} - v_{Z} - v_{BE}$	
	By applying KVL,	
	$Vo = Vin - V_{CE}$	
	Also, $V_{CE} = V_{CC} - Ic.Rc$	
	• If the input voltage Vin is increased, the output voltage Vo also increases.	
	• But this in turn makes the voltage across the emitter base junction V _{BE} to decrease.	
	If V_{BE} decreases the base current and collector current decreases which in turn	
	increases collector to emitter voltage V_{CE} . Thus reducing the output voltage V_{O} .	
	• This decrease of output voltage compensates the initial increase in output voltage.	
-1)	Thus it acts as a regulator.	48.4
d)	Derive the relationship between α and β of a transistor.	4M
Ans:	Relation between $\alpha \& \beta$:	Relati
	We know that; $I_E = I_B + I_C$ (i)	: 4M
	Dividing equation (i) by I _C .	
	$I_E / I_C = (I_B / I_C) + (I_C / I_C)$	
	Therefore, $\frac{1}{\alpha} = \frac{1}{\beta} + 1$ (Since $\alpha = I_C / I_E$, $\beta = I_C / I_B$	
	Therefore $\frac{1}{\alpha} = \frac{1+\beta}{\beta}$	
	Therefore $\alpha = \frac{\beta}{1+\beta}$	
		1

WINTER-19 EXAMINATION

Subject Code:

22216

Model Answer

		$\alpha(1+\beta) = \beta$	
		$\alpha + \alpha\beta = \beta$	
		Therefore $\alpha = \beta - \alpha\beta$ — Optional	
		Therefore $\alpha = \beta (1 - \alpha)$	
		Therefore $\beta = \frac{\alpha}{1-\alpha}$	
Q. No.	Sub Q. N.	Answers	Marking Scheme
3		Attempt any THREE of the following :	12- Total Marks
	a)	Define following parameter of rectifier:	4M
		(i) Ripple factor	
		(ii) Efficiency	
		(iii) Peak Inverse Voltage	
		(iv) Transformer utilization factor	
	Ans:	(i) Ripple Factor - Ripple factor (γ) may be defined as the ratio of the root mean	Each
		square (rms) value of the ripple voltage to the absolute value of the DC	definitio
		component of the output voltage.	n: 1M
		(ii) Efficiency- Rectifier efficiency is defined as the ratio of DC power to the applied	1
		input AC power.	
		Rectifier efficiency, η = DC output power/input AC power	
		(iii) Peak inverse voltage : For rectifier applications, peak inverse voltage (PIV) or pe	eak
		reverse voltage (PRV) is the maximum `reverse voltage that a diode can withsta	ind
		without destroying the junction	
		(iv) Transformer Utilization Factor (TUF) : Transformer Utilization Factor (TUF) is	
		defined as the ratio of DC power output of a rectifier to the effective <u>Transform</u>	<u>ier</u>
		VA rating used in the same rectifier. Effective VA Rating of transformer is the	




WINTER-19 EXAMINATION

Subject Code:

```
22216
```

Model Answer

 


WINTER-19 EXAMINATION

Subject Code:

22216

Model Answer

 



WINTER-19 EXAMINATION

Subject Code:

```
22216
```



	termed as Positive Shunt Clipper with negative Vr. The following figure represents the circuit diagram for positive shunt clipper, when the reference voltage applied is negative. V_m V_m V	
	$\begin{array}{c c c c c c c c c c c c c c c c c c c $	
	voltage, appears at the output.	
	Define with respect to FFT.	454
c)	Define with respect to FET:- (i) Static drain resistance (ii) Dynamic resistance (iii) Trans conductance (iv) Pinch-off voltage	4M
c) Ans:	(i) Static drain resistance (ii) Dynamic resistance (iii) Trans conductance	4M Each definitic n: 1M

WINTER-19 EXAMINATION

Subject Code:

22216

saturation value is called pinch off voltage.
d) State any four applications of regulated DC power supply. 4M

Q. No.	Sub Q. N.			Answers		Marking Scheme
4		Attempt any THREE o	f the following :			12- Total Marks
	(a)	Compare half wave re (i) No. of dioc (ii) Efficiency (iii) Peak invers (iv) Ripple freq	les used se voltage	vave bridge rectifier wit	th following parameters.	4M
	Ans:	PARAMETERS No. of diodes used	HWR 1	FWCR 2	FWBR 4	Four points : 4M
		Efficiency	40.6%	81.2%	81.2%	
		Peak inverse voltage	Vm	2Vm	Vm	



WINTER-19 EXAMINATION

Subject Code:

22216

	Ripple frequency	50	100	100	
(b)	Sketch the experimen	tal setup for CB trans	istor configuration.	<u> </u>	4M
Ans:	VEE	(A) $+$ E	$\begin{array}{c} BC 107 \\ C \\ B \\ C \\ C$	R _C 1.0kOhm) + V _{CC} (0-30V)	Diagram : 4M
	If α of a transistor is 0	.9, Calculate β.			4M
(c) Ans:	$ \mathbf{f} \boldsymbol{\alpha} \mathbf{o} \mathbf{f} \mathbf{a} \mathbf{transistor} \mathbf{is} 0 $ $\beta = \alpha/1 - \alpha$ $= (0.9)/(1 - 0.9)$.9, Calculate β.			4M 4M
	$\beta = \alpha/1-\alpha$.9, Calculate β.			
	$\beta = \alpha/1 - \alpha$ = (0.9)/(1-0.9)	· · ·			
Ans:	$\beta = \alpha/1 - \alpha$ = (0.9)/(1-0.9) =9	1OSFET over JFET. in either enhancemer higher input impeda n resistance due to lo acture.	nce compare to JFET. wer resistance of char		4M



WINTER-19 EXAMINATION

Subject Code:

```
22216
```

Model Answer

Ans	Block diagram of regulated DC power supply:-	Diagram : 1M
	Trans- To Ac line former Rectifier Filter Regulator Vout Load	Function : 3M
	Explanation	
	1)Transformer	
	2) Rectifier	
	3) Filter	
	4) Voltage regulator.	
	1. Transformer:- Transformer can be step up or step dow. Depending on requirement. The AC main voltage is applied to a transformer. It will increase or decrease the amplitude of ac voltage to the desired level and applies it to a rectifier.	
	2. Rectifier: The rectifier is usually a centre tapped or bridge type full wave rectifier. It	
	converts the ac voltage into a pulsating dc voltage.	
	3. Filter: The pulsating dc (or rectified ac) voltage contains large ripple. This voltage is	
	applied to the filter circuit and it removes the ripple. The function of a filter is to	
	remove the ripples to provide pure DC voltage at its output.	
	The DC output voltage thus obtained will change with the changes in load current, input voltage, etc. So it is unregulated DC voltage.	
	4. Voltage Regulator:- The unregulated DC voltage is applied to a voltage regulator. Output of the regulator circuit will be constant voltage under all operating circumstances.	
I		L



WINTER-19 EXAMINATION

Subject Code:

```
22216
```


Q. No.	Sub Q. N.	Answers	Marking Scheme
5.		Attempt any TWO of the following:	12- Total Marks
	a)	Sketch construction of N-channel JFET and explain its operating principle.	6M
	Ans:	Construction of N-channel JFET:	3M Construc tion
		P-type Channel P-type Gate Gate <	3M for operatio n principle with diagram

WINTER-19 EXAMINATION

Subject Code:

22216

Model Answer

 



WINTER-19 EXAMINATION

Subject Code:

```
22216
```

Model Answer

		This output is given to inductor, it will block ac and pass only dc.	
		This output is given to C_2 it will again bypass remaining ac and block dc ,so at output we get ripple free dc.	
-	c)	Sketch constructional diagram of LED and state its three applications.	6M
	Ans:	Emitted light P-type Active region N-type Free electron Hole Photon OR	3M for construc tional diagram 3M for applicati ons




WINTER-19 EXAMINATION

Subject Code:

22216

Model Answer

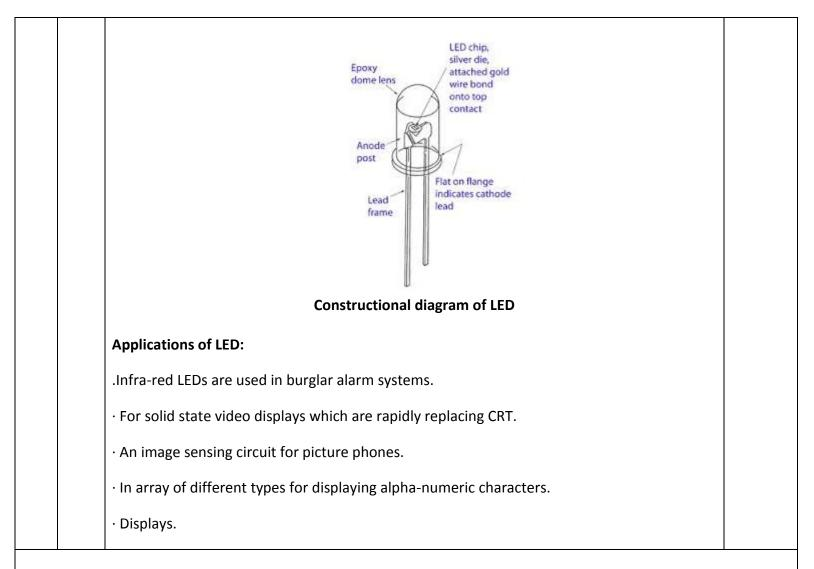

Q. No.	Sub Q. N.	Answers	Marking Scheme
6.		Attempt any TWO of the following :	12- Total Marks
	a)	Describe classification of solids on the basis of energy band diagram.	6M
	Ans:	Classification on the basis of energy theory: Based on the ability of various materials to conduct current, the materials are classified as	2M for classific ation

WINTER-19 EXAMINATION

Subject Code:

```
22216
```


Model Answer

condu	ictors, insulators and the semiconductors.
Condu	uctors
	A material having large number of free electrons can conduct very easily. For example, copper has 8.5x1028 free electrons per cubic meter which is a very large number. Hence copper is called good conductor. Intact, in the metals like copper, aluminum there is no forbidden gap between valence band and conduction band. The two bands overlap. Hence even at room temperature, a large number of electrons are available for conduction. So without any additional energy, such metals contain a large number of free electrons and hence called good conductors. An energy band diagram for a conductor is shown in the Figure (a).
Insula	tors
•	An insulator has an energy band diagram as shown in the Figure (b). In case of such insulating material, there exists a large forbidden gap in between the conduction band and the valence band. Practically it is impossible for an electron to jump from the valence band to the conduction band. Hence such materials cannot conduct and called insulators. The forbidden gap is very wide, approximately of about 7 eV is present in insulators. For a diamond, which is an insulator, the forbidden gap is about 6 eV. Such materials may conduct only at very high temperatures or if they are subjected to high voltage. Such conduction is rare and is called breakdown of an insulator. The other insulating materials are glass, wood, mica, paper etc.

WINTER-19 EXAMINATION

Subject Code:

22216

 




WINTER-19 EXAMINATION

Subject Code:

22216

 




WINTER-19 EXAMINATION

Subject Code:

22216

Model Answer

 

WINTER-19 EXAMINATION

Subject Name: Basic Electronics

Subject Code:

22216

Model Answer

a)Here R_1 and R_2 forms voltage divider biasing arrangement.

b)voltage drop across R₂, forward biases the base emitter junction.

c)so base current flows and hence collector current flows in zero signal condition.

d)R_E provides stabilization and R_C controls collector current.

It is most widely used method.

Advantages of voltage divider bias

The circuit operation is independent of the transistor current gain β .

• The resistors help to give complete control over the voltage and current.

 \cdot The emitter resistor, Re, allows for stability of the gain of the transistor, despite fluctuations in the β values.

· Operating point stabilized against shift in temperature.

 \cdot Operating point is almost independent of β variation